

C 36768



**FOURTH SEMESTER B.TECH. (ENGINEERING) DEGREE  
EXAMINATION, JUNE 2004**

CSE 404 —DIGITAL ELECTRONICS  
PTCSE 403

(Old Scheme)

Time : Three Hours

Maximum : 100 Marks

*Answer all questions.*

- I. (a) Define fan in, fan out of a logic gate.  
(b) Construct RTL - NOR gate.  
(c) What are the advantages of static RAM over dynamic RAM.  
(d) EEPROM is sometimes referred to as non-volatile RAM. Why ?  
(e) Draw the circuit of schmitt trigger.  
(f) Discuss the characteristics of Tunnel diode.  
(g) Discuss the features of programmable logic array.  
(h) Construct  $4 \times 1$  multiplexer.

(8 × 5 = 40 marks)

- II. (a) Draw the circuit of TTL gate with totem-pole output and explain the operation.

*Or*

- (b) Draw the circuit of ECL and explain the operation.

- III. (a) A computer uses RAM chips of  $1024 \times 1$  capacity. How many chips are needed and how should their address lines be connected to provide a memory capacity of 1024 bytes ?

*Or*

- (b) Draw the circuit of dynamic RAM (CMOS) and explain its function.

- IV. (a) Draw the circuit of emitter coupled monostable multivibrator and explain the operation with suitable waveforms.

*Or*

- (b) Discuss the principle behind UJT. Give the constructional details. Draw the characteristics and explain.

- V. (a) Implement the following Boolean function with a  $4 \times 1$  multiplexer and external gates. Connect inputs A and B to the selection lines. The input requirements for the four data lines will be a function of variables C and D.

$$F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$$

*Or*

- (b) Construct  $5 \times 32$  decoder with four  $3 \times 8$  decoders with enable and one  $2 \times 4$  decoder.

(4 × 15 = 60 marks)