

**THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE
EXAMINATION, JANUARY 2003**

EC2K. 302. ELECTRICAL CIRCUITS AND NETWORK THEORY

(New Scheme)

Time : Three Hours

Maximum : 100 Marks

Answer all questions.

1. (a) Name the various types of sources and explain.
- (b) State and explain maximum power transfer theorem.
- (c) State and prove initial value theorem.
- (d) Find the inverse Laplace transform of the function $F(s) = \frac{1}{(s-a)^2}$, using convolution theorem.
- (e) Express y -parameters in terms of z -parameters.
- (f) The network N of the figure 1 is terminated at port 2 in impedance $Z_L = \frac{1}{y_L}$. Show that the transfer impedance for the combination is $Z_{12} = \frac{z_{21}Z_L}{z_{22} + Z_L}$.

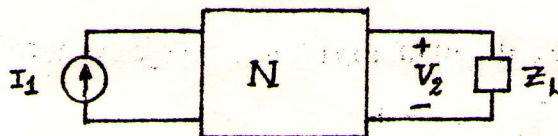


FIG. 1.

- (g) Explain the properties of positive Real functions.
- (h) State and explain Sturm's theorem.

(8 × 5 = 40 marks)

2. (a) (i) In the network of the figure, a steady state is reached with switch K open. At $t = 0$, switch K is closed. Find $i(t)$, sketch the current waveform and indicate the value of the time constant.

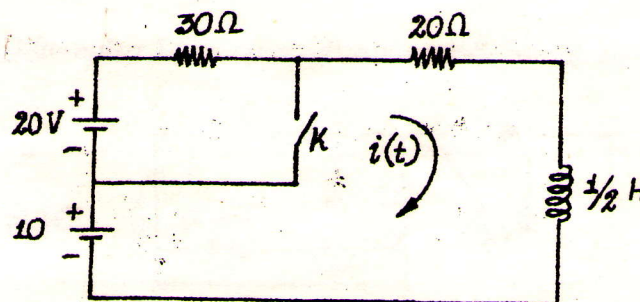


FIG. 2.

(8 marks)

Turn over

- (ii) For the network shown in figure, prove that $V_0 = \frac{V_1}{2} (1 + a + b - ab)$ and $Z_0 = \frac{3-b}{2}$.

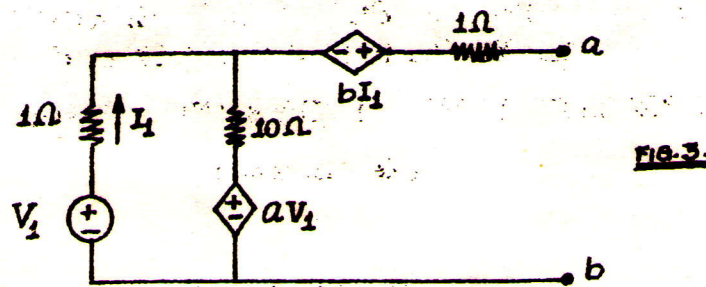


FIG. 3.

(7 marks)

Or

- (b) (i) Determine the Norton equivalent network for the terminals acts in the figure for zero initial condition.

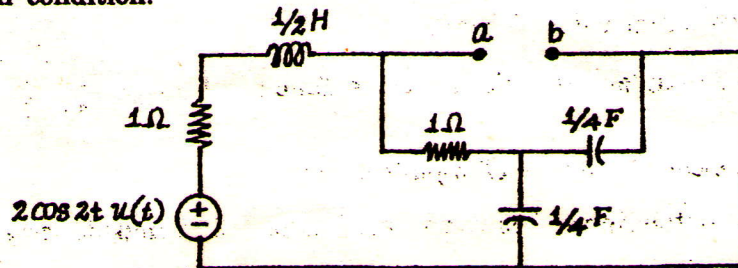


FIG. 4.

(7 marks)

- (ii) In the given network, the $10 \mu\text{F}$ capacitor is charged to 1000 V and switch K is closed at $t = 0$. Solve for $\frac{d^2 i_2}{dt^2}$ at $t = 0^+$.

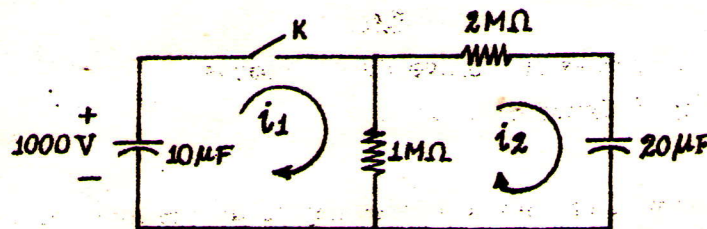


FIG. 5.

(8 marks)

3. (a) (i) In the network of the figure, determine the numerical value of i_1 .

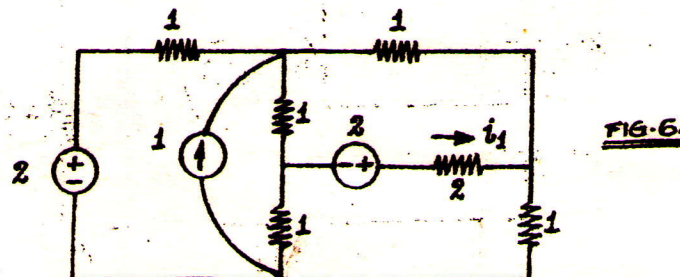


FIG. 6.

(7 marks)

- (ii) In the network shown, the switch K is closed at $t = 0$. Show that current $i(t)$ is given by the equation

$$i(t) = \frac{V}{Z} \sin(\omega t - \phi) + \frac{WL V}{Z^2} e^{-Rt/L}$$

where $Z = \sqrt{R^2 + (WL)^2}$ and $\phi = \tan^{-1} \frac{WL}{R}$.

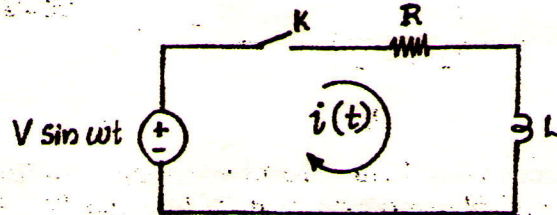


FIG. 7.

(8 marks)

Or

- (b) (i) What must be the relationship between L_{eq} and L_1 , L_2 and M for networks to be equivalent?

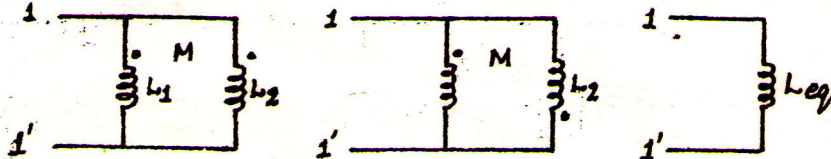


FIG. 8.

(7 marks)

- (ii) Show that with $Z_a Z_b = R_0^2$ in the Bridged T-network of the figure.

$$\frac{V_2}{V_1} = \frac{1}{1 + Z_a / R_0}$$

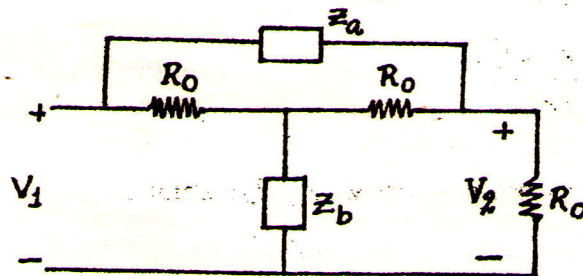


FIG. 9.

(8 marks)

4. (a) (i) Find y and z parameters for the network shown in figure.

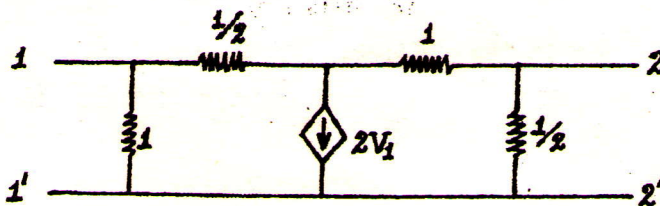


FIG. 10.

(8 marks)

Turn over

- (ii) The network N in the Fig. may be described by the z parameters. Show that with port 2 open, $G_{12} = \frac{z_{21}}{z_{11}}$.

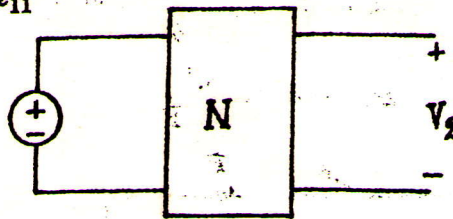


FIG. 11

(7 marks)

Or

- (b) (i) Design a constant K, T section high pass filter having $f_C = 10$ kHz and $R_0 = 600 \Omega$. Also find (1) its Z_{OT} and phase constant at 25 kHz and (2) attenuation at 5 kHz. (8 marks)
- (ii) For the two networks shown in Fig., show that the two networks are equivalent if $Y_a = Z_2/D$, $Y_b = Z_2/D$ and $Y_c = Z_1/D$, where $D = Z_1Z_2 + Z_2Z_3 + Z_3Z_1$.

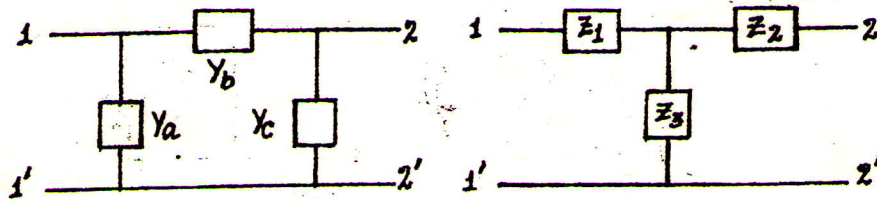


FIG. 12

(7 marks)

5. (a) (i) Test each of the functions for positive real function :

(1) $\frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$

(2) $\frac{2s^3 + s^2 + 4s + 1}{s^3 + 3s^2 + 3s + 1}$

(8 marks)

- (ii) Explain the properties of Hurwitz polynomials.

(7 marks)

Or

- (b) Obtain all the Foster and Cauer realizations of the driving point function

$$Z(s) = \frac{(s+1)(s+4)}{(s+3)(s+5)}$$

(15 marks)

[4 × 15 = 60 marks]