

D 30340

(Pages : 4)

Name.....

Reg. No.....

THIRD SEMESTER B.TECH. DEGREE EXAMINATION, DECEMBER 2003

IT/CS 2K 306/PTCS2K 305. ELECTRIC CIRCUIT SYSTEM

Time : Three Hours

Maximum : 100 Marks

1. (a) Use initial value theorem and final value theorem to find $f(0)$ and $f(\infty)$ if $F(s) = (s+2)/s(s+3)(s+4)$.
- (b) Two coupled coils are connected in parallel as shown in the Fig. 1. Derive an expression for equivalent inductance.

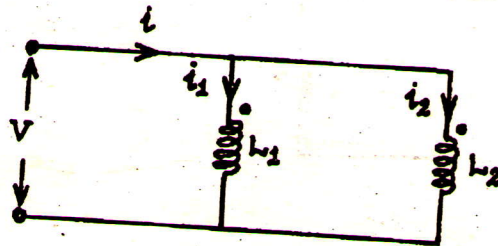


Fig. 1.

- (c) State, explain and illustrate compensation theorem.
- (d) Find image parameters for the network shown in the Fig. 2.

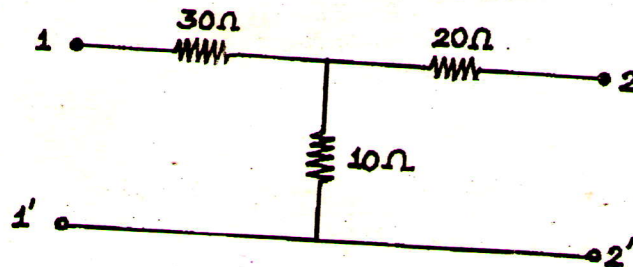


Fig. 2.

- (e) Find the transform admittance of the network shown in the Fig. 3.

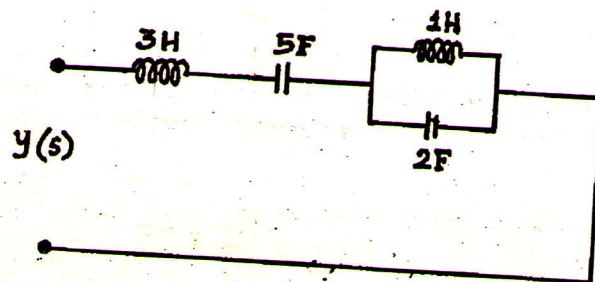


Fig. 3.

- (f) Define gain margin and phase margin.
- (g) What is Nichol's chart? What are the advantages of Nichol's chart over the M and N circles?

Turn over

- (h) The unity feedback system has a open-loop transfer function of

$$G(s) = 25(s+4)/s(s+0.5)(s+2).$$

Find the steady state error for unit ramp input and for parabolic input.

(8 × 5 = 40 marks)

2. (a) Solve for the current I_1 shown in the network of the Fig. 4.

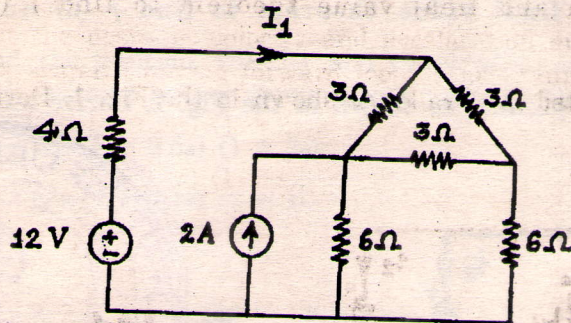


FIG. 4.

Or

- (b) Obtain the dotted equivalent circuit for the coupled circuit shown in the Fig. 5 and use it to find the voltage V across the 10Ω capacitive reactance.

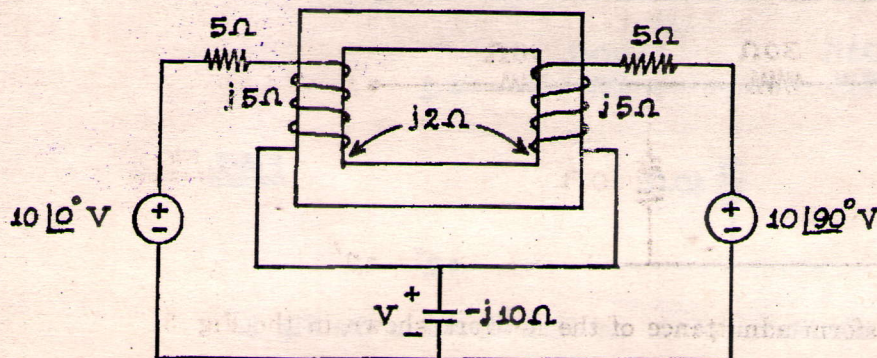


FIG. 5.

(15 marks)

3. (a) (i) In the single source network shown in the Fig. 6 the voltage source cause a current of I_x in the 4Ω branch. Find I_x and then verify the reciprocity theorem.


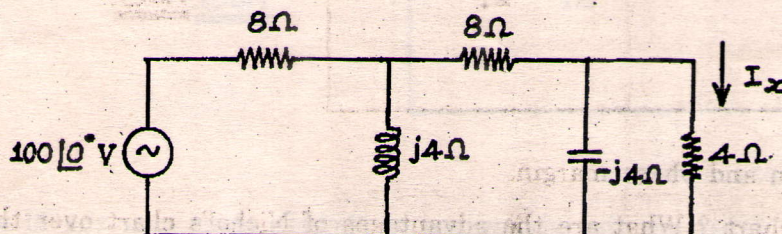


FIG. 6.

(7 marks)

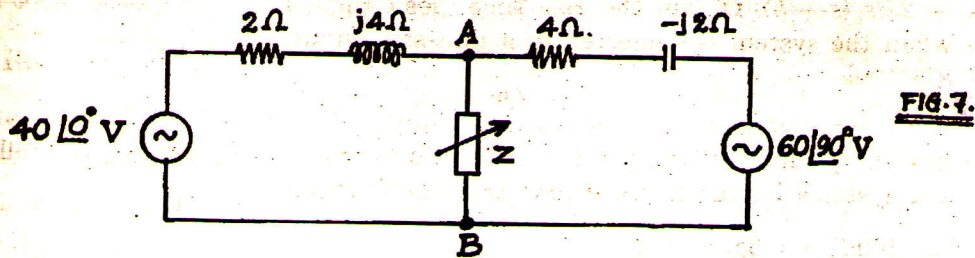
- (ii) In the network shown in the Fig. 7 the impedance Z connected across AB is variable in both resistance and reactance. What load impedance Z will receive maximum power? What is the value of the maximum power?



(8 marks)

Or

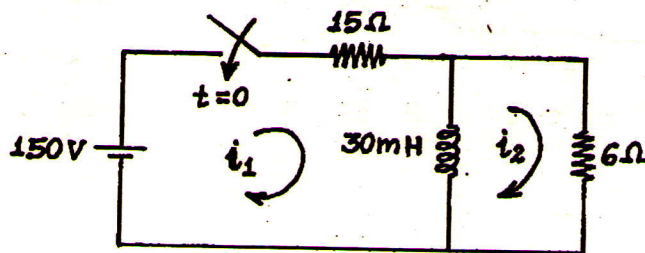
- (b) In the circuit of Fig. 8 find the initial and final values of I_1 and I_2 (using initial and final value theorems), when switch is closed.



(15 marks)

4. (a) Refer to the two port network shown in the Fig. 9 and find

- (i) h parameters.
- (ii) z parameters.

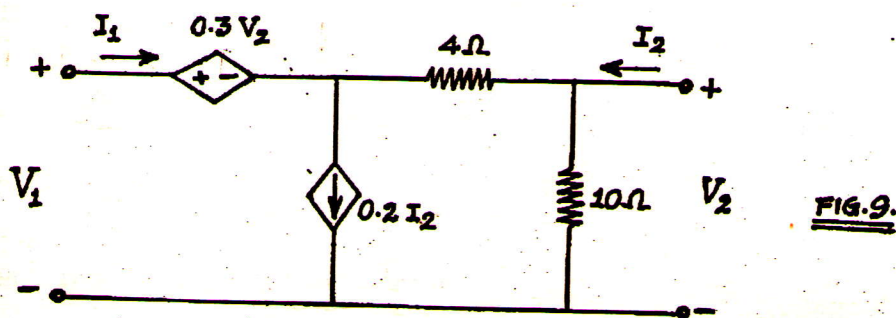

Or

Turn over

- (b) Explain the principle and the method of using Anderson's bridge in bridge circuits. (15 marks)
5. (a) Consider the unity feedback closed loop system where the forward transfer function is $G(s) = 25/s(s + 5)$. Obtain the rise time, peak time, maximum over shoot and settling time when the system is subjected to a unit-step input.

Or

- (b) Find out the position, velocity and acceleration error coefficients for the following unity feedback systems having forward loop transfer function $G(s)$ as :
- (i) $100/(1 + 0.5s)(1 + 2s)$.
- (ii) $K/s(1 + 0.1s)(1 + s)$.

(15 marks)

[4 × 15 = 60 marks]