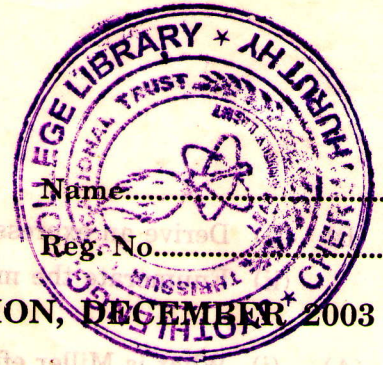


D 30342

(Pages : 2)



Name.....

Reg. No.....

**THIRD SEMESTER B.TECH. DEGREE EXAMINATION, DECEMBER 2003**

**EE.2K. 304. ELECTRONICS—I**

Time : Three Hours


Maximum : 100 Marks

*Answer all the questions.*

- I. (a) Distinguish the Electrical properties of Silicon from germanium.  
(b) Explain how a PN junction diode can be used as an electronic switch.  
(c) What is d.c. load line ? Explain how Q-point is fixed on d.c. load line.  
(d) Write clamping circuit theorem. Enumerate its applications in Communication Engineering.  
(e) What is thermal runaway ? What are methods to combat thermal runaway ? Explain.  
(f) Distinguish class B from class AB operation.  
(g) Define and explain :  
(i) Gain.  
(ii) Bandwidth.  
(iii) Frequency response.  
(h) Define and explain Gain bandwidth product of an amplifier. (8 × 5 = 40 marks)
- II. (A) (i) Show the potential variations within step and graded semiconductors.  
(ii) Explain how a P-N junction can be used as a rectifier. (8 + 7 = 15 marks)
- Or*
- (B) Distinguish JFET from BJT. Explain the construction and characteristics of JFET with neat diagrams. Derive the relationship among FET parameters. (15 marks)
- III. (A) (i) Write a note on a.c. load line.  
(ii) Compare and contrast the parameters of full wave centre-tapped rectifier from bridge rectifier. (8 + 7 = 15 marks)
- Or*
- (B) What are the types of limiters ? Explain the operation of each type in detail. (15 marks)
- IV. (A) (i) What is fixed bias ? Explain. Derive the Q-point parameters for a fixed bias circuit.  
(ii) Bring out the advantages of *h*-parameter model of a BJT. (8 + 7 = 15 marks)

*Or*

**Turn over**

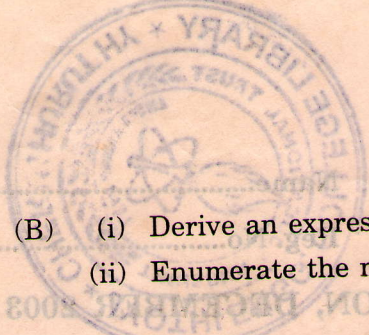

- (B) (i) Derive an expression for the voltage gain of a common source FET amplifier.  
(ii) Enumerate the methods of biasing JFET. (8 + 7 = 15 marks)
- V. (A) (i) What is Miller effect ? Give the advantages and applications of this effect. Show the application of this effect using an example.  
(ii) Derive the parameters of Emitter follower at high frequencies. (8 + 7 = 15 marks)

Or

- (B) (i) Enumerate the importance of CMRR for a differential amplifier. (8 + 7 = 15 marks)  
(ii) Explain the types of differential amplifier. [4 × 15 = 60 marks]

(8 × 5 = 40 marks)

(8 + 7 = 15 marks)

(15 marks)

(8 + 7 = 15 marks)

(15 marks)

(8 + 7 = 15 marks)

Turn over