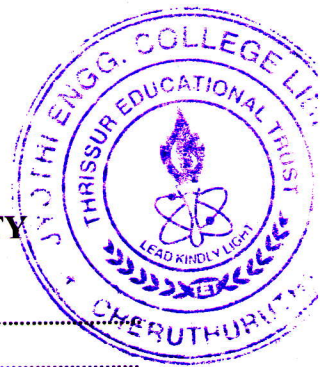


APJ ABDULKALAM TECHNOLOGICAL UNIVERSITY  
08 PALAKKAD CLUSTER



Q. P. Code : PE0820321B-I

(Pages: 2)

Name: .....

Reg. No: .....

THIRD SEMESTER M.TECH. DEGREE EXAMINATION FEBRUARY 2021

Branch: Electrical & Electronics Engineering

Specialization: Power Electronics

08EE7221 (B): Design of Power Electronics System

(Common to PE)

Time: 2 hour 15 minutes

Max. marks: 60

Answer all six questions.


Modules 1 to 6: Part 'a' of each question is compulsory and answer either part 'b' or part 'c' of each question.

Q.no.	Module 1	Marks
1.a	What is the need for electrical isolation in drive circuits	3
	<b>Answer b or c</b>	
b	Explain the design procedure for dc coupled drive circuits with unipolar output with the help of neat diagram	6
c	What are the practical considerations in the design and fabrication of drive circuits for the successful operations	6
Q.no.	Module 2	Marks
2.a	Why snubbers are used with transistors? List out the types of snubber circuits.	3
	<b>Answer b or c</b>	
b	Discuss the design procedure for a turn off snubber circuit for transistor	6
c	Analyse the effect of adding a snubber resistance to capacitor snubber	6
Q.no.	Module 3	Marks
3.a	What are the factors to be considered while designing a snubber circuit for GTO	3
	<b>Answer b or c</b>	
b	Discuss the steps for the design of an overvoltage snubber	6
c	What are the points to be considered while designing a snubber for GTO	6

Q.no.	Module 4	Marks
4.a	Discuss about the heat transfer by conduction	3

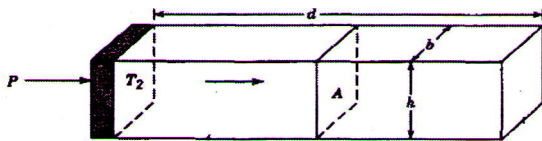**Answer b or c**

- b** A transistor module is mounted on an aluminium plate having dimensions  $h=4\text{cm}$ ,  $b=5\text{cm}$  and  $d=3\text{mm}$ . A temperature drop of  $4^\circ\text{C}$  is allowed from one  $4 \times 5\text{ cm}^2$  surface to the other. Find the maximum power that can be generated in the module. Ignore any heat losses to the surrounding air



- c** What are the factors to be considered while selecting a proper heat sink. Also write the design equations

Q.no.	Module 5	Marks
5.a	Explain about the generation of electromagnetic interference in power converters	4

**Answer b or c**

- b** What is a common mode choke and explain its various modes of operation? Discuss about any one application of it
- c** What is stray capacitance? What is its effect on power electronic circuits?

Q.no.	Module 6	Marks
6.a	Discuss about the frequency response of series resonant inverters with figures	4

**Answer b or c**

- b** Derive the equation for current through inductor in series resonant circuit with capacitor parallel load
- c** A series resonance inverter with parallel-loaded delivers a load power of  $P_L = 1\text{kW}$  at a peak sinusoidal load voltage of  $V_p = 330\text{V}$  and at resonance. The load resistance is  $R = 10\ \Omega$ . The resonant frequency is  $f_0 = 20\text{kHz}$ . Determine (a) the dc input voltage  $V_s$ , (b) the frequency ratio  $u$  if it is required to reduce the load power to  $250\text{ W}$  by frequency control, (c) the inductor  $L$ , and (d) the capacitor  $C$ .