

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree (S,FE) Examination December 2020 (2015 Scheme)

Course Code: EC209**Course Name: ANALOG ELECTRONICS (MC)**

Max. Marks: 100

Duration: 3 Hours

**PART A***Answer all questions, each carries 5marks.*

Marks

- | | | |
|---|--|-----|
| 1 | Explain the load line concept of a diode. | (5) |
| 2 | Make a short note on the operating point of BJT. | (5) |
| 3 | Distinguish the different types of MOSFET. | (5) |
| 4 | Write a short note on Darlington pair. | (5) |
| 5 | Explain the operation of a Colpitts oscillator with the help of a diagram. | (5) |
| 6 | Describe the operation of a monostable multivibrator using transistors. | (5) |
| 7 | Draw the functional diagram of 555 timer IC. | (5) |
| 8 | Discuss the working of a UJT as an oscillator. | (5) |

PART B*Answer any three questions, each carries 10 marks.*

- | | | |
|----|--|------|
| 9 | a) Explain the working of any one of the clamping circuits with suitable diagrams. | (5) |
| | b) Derive the equation for the ripple factor of a full wave rectifier. | (5) |
| 10 | a) Why do gain falls at low frequencies and high frequencies in the amplifiers? | (5) |
| | b) What are cascaded amplifiers? | (5) |
| 11 | a) What are the effects of a negative feedback? | (4) |
| | b) Describe the drain characteristics of JFET. | (6) |
| 12 | Explain briefly the principle of Class AB amplifier with the help of suitable diagrams. | (10) |
| 13 | a) Draw h parameter model of BJT and derive the expressions for voltage gain and current gain. | (7) |
| | b) Why is biasing required in transistors? | (3) |

PART C*Answer any two questions, each carries 15 marks.*

- | | | |
|----|---|-----|
| 14 | a) With the help of a circuit diagram derive the frequency of oscillation for Hartley oscillator. | (7) |
| | b) State the Barkhausen criteria for oscillations. | (3) |
| | c) Explain in detail about the operation of astable multivibrator using transistors. | (5) |

- 15 a) Write a short note on the different classifications of oscillators. (5)
b) Derive frequency of oscillation for RC phase shift oscillator with the help of a circuit diagram. (10)
- 16 a) Explain the concept of offline UPS. (5)
b) Write in brief about astable multivibrator using 555 timer IC. (10)
- 17 a) Write in detail about the operation of a SMPS. (5)
b) Explain the principle of PLL in detail. (5)
c) Discuss in detail about the lock range and capture range. (5)
