

C

0800ITT203122001



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree Examination December 2020 (2019 Scheme)

Course Code: ITT203

Course Name: DIGITAL SYSTEM DESIGN

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions. Each question carries 3 marks

Marks

- 1 Determine the base of the numbers in the following operations: (3)
 - a) $31 / 2 = 13$
 - b) $104 + 117 = 223$
- 2 Using 8-bits, give the 1's and 2's complement representation of the following decimal numbers. (3)
 - a) +54
 - b) -68
- 3 Draw the truth table for the function $F(x,y,z) = xyz' + x'y'$. (3)
- 4 The product of all minterms of a Boolean function of n variables is 0. Prove the above statement for n=2. (3)
- 5 Construct a 4 X 16 decoder with two 3 X 8 decoders. (3)
- 6 Design and implement a half subtractor. (3)
- 7 Differentiate between a latch and a flip flop. Draw the logic diagram of D-latch and D- flip-flop. (3)
- 8 Derive the characteristic table and characteristics equations of D, JK and T flip-flops. (3)
- 9 Differentiate between RAM and ROM. (3)
- 10 Explain PLA with a block diagram. (3)

PART B

Answer any one full question from each module. Each question carries 14 marks

Module 1

- 11 a) Represent the decimal digits (0 to 9) using BCD, 2421 code, gray code and excess-3 code. (8)

0800ITT203122001

- b) Perform the following operations (6)
- i) $(367)_8 + (175)_8$
 - ii) $(1A36)_{16} + (37E1)_{16}$
 - iii) $(162)_8 - (457)_8$
- 12 a) Represent the unsigned decimal numbers 786.25 and 232.58 in BCD. (8)
Show the necessary steps to find their sum and difference.
- b) Perform the following base conversions. (6)
- i) $(4A10)_{16}$ to Octal
 - ii) $(91.60)_{10}$ to binary
 - iii) $(132)_4$ to decimal

Module 2

- 13 a) Minimize the Boolean function $F(A,B,C,D) = \Sigma (0,1,5,7,8,9,10,11,14,15)$ (10)
using McClusky minimization technique.
- b) Express the following Boolean functions:
- i) $F_1(A,B,C,D) = AC + B'D + CD'$ in sum of Minterms form.
 - ii) $F_2(A,B,C,D) = C(A+B'+D)(B'+C')$ in product of Maxterms form. (4)
- 14 a) Simplify the given Boolean function and don't care condition using K-map (7)

$$F(w,x,y,z) = w'(x'y + x'y') + x'z'(y + w)$$

$$d(w,x,y,z) = w'x(y'z + yz) + wyz$$

- b) Simplify the given Boolean function using K- Map and obtain the simplified expression in SOP and POS forms.

$$F(A,B,C,D) = \Sigma_m(0,2,4,5,7,13,14) + \Sigma_d(3,6,12,15) \quad (7)$$

Module 3

- 15 Design a 4-bit Gray to Binary code converter. (14)
- 16 a) What is a multiplexer? Draw the logic diagram of a 4X1 multiplexer, (5)
clearly indicating the inputs and outputs.
- b) Implement the function $F(A,B,C,D) = \Sigma(0,3,5,7,9,12,13)$ using (9)
- i) 8 X 1 MUX
 - ii) 4 X 1 MUX

Module 4

- 17 a) Draw the circuit of clocked RS flip flop using NAND gates. Obtain the (5)
characteristic table and characteristic equations also.
- b) Design JK Flip Flop by using SR Flip Flop (9)

- 18 a) Compare Synchronous and Asynchronous sequential circuits. (4)
- b) A sequential circuit has two flip flops (A and B), one input (x) and one output (z). The flip flop input functions and the circuit output functions are as follows. (10)

$$\begin{aligned}JA &= xB+B' & KA &= xB' \\JB &= xA' & KB &= x+A \\z &= xA + x'B\end{aligned}$$

Obtain the state table, state diagram and state equations.

Module 5

- 19 a) Draw the circuit of a 4-bit synchronous binary counter and explain its working. (5)
- b) Design a serial adder using a sequential logic procedure. (9)
- 20 a) Draw and explain 4 bit Johnson counter. Also draw its timing sequence. (7)
- b) Implement a 4- bit bidirectional shift registers with parallel load and explain its working. (7)
