



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Fourth Semester B.Tech Degree (S,FE) Examination August 2021 (2015 Scheme)

Course Code: EC212**Course Name: LINEAR INTEGRATED CIRCUITS AND DIGITAL ELECTRONICS (MC)**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer all the questions below; each one carries 5 marks.*

- | | Marks |
|---|-------|
| 1 Define the following terms and explain their significance in practical circuits | (5) |
| (i) Input offset current | |
| (ii) Slew rate | |
| 2 How can we clip the positive half cycle of a signal using op amp. | (5) |
| 3 Discuss briefly about wide band pass filter. | (5) |
| 4 State and prove the De Morgan's Theorem. | (5) |
| 5 Design and implement a full adder with minimum number of gates. | (5) |
| 6 Compare the characteristics of SRAM and DRAM. | (5) |
| 7 Design a 4-bit ring counter using D flip flop. | (5) |
| 8 Elaborate the importance of master-slave FFs with an example. | (5) |

PART B*Answer any three full questions; each carries 10 marks.*

- | | |
|---|------|
| 9 With the help of a neat diagrams, show that op amp can be used as integrator and differentiator | (10) |
| 10 (a) Explicate the threshold levels of a regenerative comparator with necessary diagrams. | (5) |
| (b) Draw the circuit diagram and waveform of a Sample & Hold circuit using op-amp. Explain its working. | (5) |
| 11 (a) Illustrate the working principle of an 8-bit successive approximation A/D converter. | (6) |
| (b) Distinguish Butterworth filter from Chebyshev filter. | (4) |
| 12 Minimize the following function using Karnaugh map and implement using basic logic gates. | (10) |

$$F(A,B,C,D) = \sum m(0,1,3,5,7,8,9,11,13,15)$$

- 13 Elucidate the working of an Astable multivibrator with a circuit diagram and waveform. (10)

PART C

Answer any two full questions; each carries 15 marks.

- 14 Summarize the following (15)
- (i) synchronous up counter
 - (ii) synchronous down counter
- 15 Design and implement a 3-bit binary to grey code converter. (15)
- 16 Design the following (15)
- a) octal to binary encoder
 - b) 3-to-8 decoder.
- 17 Discuss in detail about JK flip flop and obtain the characteristic equation of JK flip flop. (15)
