

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Seventh Semester B.Tech Degree (Hons.) Examination December 2021 (2015 Scheme) (2018 admn.)

**Course Code: EC461****Course Name: MICROWAVE DEVICES AND CIRCUITS**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer any two full questions, each carries 15 marks.*

Marks

- 1 a) What are the Characteristics and advantages of microwaves? (5)
- b) With neat diagram and governing equations explain Ridley-Watkin-Hilsum theory. (10)
- 2 a) A certain GaAs MESFET has the following parameter (3)
- Channel height 'a' = 0.1 μm
- Electron concentration, $N_d = 8 \times 10^{17}/\text{cm}^3$
- Relative dielectric constant, $\epsilon_r = 13.10$
- Calculate Pinch-off voltage (V_p) ?
- b) Derive the expression for available power gain of microwave amplifier. (7)
- c) Design a negative resistance microwave oscillator. (5)
- 3 a) What does TRAPATT stands for? With neat diagram explain the construction and working of it. (7)
- b) What is MESFET ? Mention its structure and operation. (8)

PART B*Answer any two full questions, each carries 15 marks.*

- 4 a) Convert S-matrix into Z-matrix. (7)
- b) Discuss the working of quarter wave transformer and half wave transformer (8)
- 5 a) What are the steps required to transfer a LPF to HPF, explain. (8)
- b) Explain working of Double Stub tuning (7)
- 6 a) List the Kuroda Identity. (5)
- b) Design a low-pass composite filter with a cut-off frequency of 3 MHz and impedances of 75Ω . (10)

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Explain in detail about thick film and thin film technology? (10)
b) Discuss in detail about the various losses in microstrip lines. (5)
c) Discuss briefly about slot line. (5)
- 8 a) Compare Monolithic MICs with hybrid MICs (10)
b) Discuss discontinuities in MICs. (5)
c) With neat diagram explain SPDT Transmit – Receive switch. (5)
- 9 a) Explain the working and applications of Circulators and Isolators. (10)
b) Explain the frequency characteristics of single layer square inductor. (5)
c) Explain the configuration of Planar capacitor film. (5)
