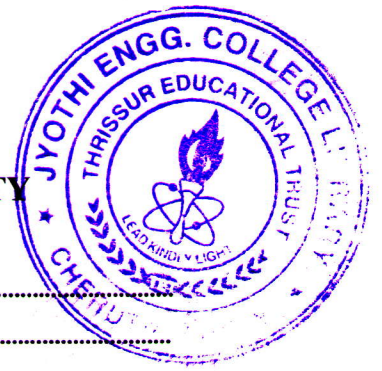


APJ ABDULKALAM TECHNOLOGICAL UNIVERSITY
08 PALAKKAD CLUSTER



Q. P. Code: PE0821321B-I

(Pages: 2)

Name:

Reg. No:

THIRD SEMESTER M.TECH. DEGREE EXAMINATION DECEMBER 2021

Branch: Electrical and Electronics Engineering

Specialization: Power Electronics

08EE7221(B) DESIGN OF POWER ELECTRONICS SYSTEM

(Common to PE)

Time: 3 hours

Max. Marks: 60

Answer all six questions.

Modules 1 to 6: Part 'a' of each question is compulsory and answer either part 'b' or part 'c' of each question.

Q. No.	Module 1	Marks
1.a	What is the need for electrical isolation in drive circuits.	3

Answer b or c

- | | | |
|---|--|---|
| b | Explain the design procedure for cascade drive circuits for normally on power devices with the help of neat diagram. | 6 |
| c | Explain the design procedure for dc coupled drive circuits with unipolar output with the help of neat diagram. | 6 |

Q. No.	Module 2	Marks
2.a	SCR is operated with a supply voltage of 400V. The dv/dt is 500V/us and di/dt is 20A/us. Calculate the value of snubber circuit parameters and inductance for a damping ratio of 0.5.	3

Answer b or c

- | | | |
|---|---|---|
| b | Discuss the design procedure for a turn-off snubber circuit for transistor. | 6 |
| c | Design the values of di/dt inductor and RC snubber components for the SCR working in a 230V system. Given di/dt rating is 90A/us and dv/dt rating is 200V/us. Effective series resistance is 1.5ohm. Take the damping ratio as 0.6. | 6 |

Q. No.	Module 3	Marks
3.a	What are the factors to be considered while designing a snubber circuit for GTO	3

Answer b or c

- | | | |
|---|--|---|
| b | Discuss the design procedure for a turn-off snubber circuit for GTO. | 6 |
|---|--|---|


- c Discuss the steps for the design of an overvoltage snubber. 6

Q. No. Module 4 Marks

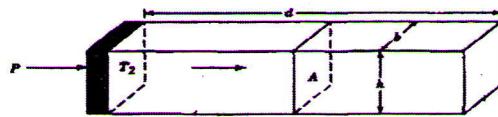- 4.a Discuss about heat transfer by convection 3

Answer b or c

- b A transistor module is mounted on an aluminium plate having dimensions $h=4\text{cm}$, $b=5\text{cm}$ and $d=3\text{mm}$. A temperature drop of 4°C is allowed from one $4 \times 5\text{ cm}^2$ surface to the other. Find the maximum power that can be generated in the module. Ignore any heat losses to the surrounding air. 6



- c Find $R_{e,rad}$ for a cube of black oxidised aluminium 10 cm on a side. Assume $T_s = 120^\circ\text{C}$ and $T_a = 20^\circ\text{C}$ 6

Q. No. Module 5 Marks

- 5.a Explain about the generation of electromagnetic interference in power converters 4

Answer b or c

- b What is stray capacitance? What is its effect on power electronic circuit? 8
- c What is a common mode choke and explain its various modes of operation? Discuss about any one application of it. 8

Q. No. Module 6 Marks

- 6.a Explain in detail about the zero voltage switching in resonant converter. 4

Answer b or c

- b Derive the equation for current through inductor in series resonant circuit with capacitor parallel load. 8
- c A series resonance inverter with parallel-loaded delivers a load power of $P_L=1\text{ kW}$ at a peak sinusoidal load voltage of $V_p = 330\text{V}$ and at resonance. The load resistance is $R = 10\text{ ohm}$. The resonant frequency is $f_o=20\text{kHz}$. Determine (a) the dc input voltage V_s (b) the frequency ratio u if it is required to reduce the load power to 250 W by frequency control (c) the inductor L and (d) the capacitor C . 8