


Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

0800RAT203122002

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

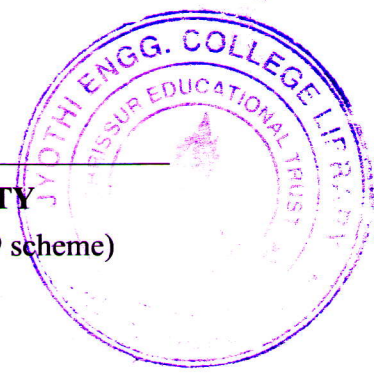Third Semester B.Tech Degree Examination December 2021 (2019 scheme)



Course Code: RAT203

Course Name: ELECTRONIC DEVICES AND CIRCUITS

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer all questions. Each question carries 3 marks*

Marks


- 1 Design a clipping circuit to clip a sine wave at  $\pm 4V$ . (3)
- 2 Briefly explain the working of zener shunt voltage regulator. (3)
- 3 Explain how FET will function as a switch. (3)
- 4 Draw the hybrid pi model of BJT amplifier. (3)
- 5 Differentiate between positive and negative feedback. (3)
- 6 What is cross over distortion? How it can be eliminated? (3)
- 7 What is the working principle of an oscillator? (3)
- 8 Compare an ideal op-amp and practical op-amp. (3)
- 9 Draw and explain the working of a basic integrator circuit using op-amp. (3)
- 10 Define lock range and capture range of PLL. (3)

**PART B**

*Answer any one full question from each module. Each question carries 14 marks*

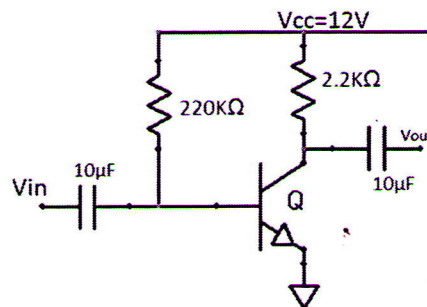**Module 1**

- 11 a Explain bias compensation using diode and thermistor (6)
- b Calculate the input resistance, output resistance and voltage gain for the circuit shown using h parameter model. (8)



- 12 a Sketch and explain the circuit of a double ended clipper using ideal PN diodes which limits the output between  $\pm 6V$  for an input of  $\pm 10V$ . Also draw the transfer characteristics. (7)

**0800RAT203122002**

- b For the fixed bias circuit,  $V_{CC}=10V$ ,  $R_B=50K\Omega$ ,  $R_C=500\Omega$ , find the operating point and locate the operating point on the dc load line. Assume silicon transistor with  $\beta=50$  and  $V_{BE}=0.7V$  (7)

**Module 2**

- 13 a With the aid of drain and transfer characteristics, explain the working of n-channel enhancement MOSFET (8)
- b For a JFET using voltage divider bias,  $R_1=12K\Omega$ ,  $R_2=4K\Omega$ ,  $R_D=500\Omega$ ,  $R_S=1K\Omega$ . Calculate the voltage at i) the gate ii) the source iii) the drain iv) from drain to source. (6)
- 14 a Discuss the low frequency analysis of FET common source amplifier. (8)
- b What is Miller's theorem. Explain the significance of Miller effect capacitance. (6)

**Module 3**

- 15 a Compare RC coupled and transformer coupled amplifiers. (6)
- b Explain the effect of negative feedback on gain, input impedance, output impedance and bandwidth of an amplifier. (8)
- 16 a Discuss the basic feedback topologies with respect to gain, input impedance and output impedance. (8)
- b Discuss the operation of series fed class A power amplifier. Write the conversion efficiency. (6)

**Module 4**

- 17 a With a neat circuit diagram, explain the working of Hartley oscillator. Also derive an expression for frequency of oscillation. (8)
- b Explain the working of a non-inverting amplifier using op-amp. Derive the expression for closed loop voltage gain. (6)
- 18 a Draw the equivalent circuit of ideal and practical op-amp. (4)
- b Define (i) Input bias current (ii) Slew rate (iii) Input offset voltage (iv) CMRR (6)
- c Explain the working principle of crystal oscillator. (4)

**Module 5**

- 19 a Draw and explain the working of instrumentation amplifier. Also derive the expression for gain. (7)
- b Write short note on 78XX and 79XX voltage regulators. (3)
- c Explain the effect of slew rate on waveform generation. (4)
- 20 a Explain the working of Astable multivibrator using 555 Timer IC with relevant waveforms and functional diagram (8)
- b With a neat functional diagram, explain the operation of IC 723. (6)

\*\*\*\*\*