

B

02000EC212062201

Pages: 2

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
Fourth Semester B.Tech Degree (S,FE) Examination June 2022 (2015 scheme)



Course Code: EC212

Course Name: LINEAR INTEGRATED CIRCUITS AND DIGITAL ELECTRONICS
(MC)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks.

Marks

- 1 Explain inverting and non-inverting amplifier in terms of gain, circuit diagram, and waveform. (5)
- 2 What is the operating principle of an isolation amplifier? Write any two applications of it. (5)
- 3 Analyse a 2-bit flash ADC with its circuit diagram. (5)
- 4 State and prove De-Morgan's Theorem. (5)
- 5 Design and implement a full adder circuit. (5)
- 6 Distinguish static and dynamic RAM. (5)
- 7 Discuss the need of a master slave JK flip-flop with circuit diagram. (5)
- 8 Illustrate SIPO and PIPO shift registers. Mention their characteristics. (5)

PART B

Answer any three full questions, each carries 10 marks.

- 9 a) Design a circuit to obtain a triangular waveform if the given input signal is sinusoidal. (10)
- 10 a) Design a Schmitt trigger of threshold voltage value $\pm 3v$. (10)
- 11 a) Elucidate a second order low pass filter with its circuit diagram, gain, cut-off frequency and frequency response. (10)
- 12 a) Minimize the expression using K Map (8)
 $F(A, B, C, D) = m(1, 2, 6, 7, 13, 14, 15) + d(3, 5, 12)$
b) Explain the significance of Don't care conditions. (2)
- 13 a) Discuss on successive approximation ADC. (10)

PART C

Answer any two full questions, each carries 15 marks.

- 14 a) Elaborate on an 8 x 1 multiplexer. (15)
- 15 a) Design a 4-bit gray –binary code converter. (15)
- 16 a) Explicate a 3- bit synchronous down counter using T flip-flop. (15)
- 17 a) Explain a Mealy sequence detector with an example. (15)
