

B

02000ECT202052104



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
Fourth Semester B.Tech Degree Examination June 2022 (2019 scheme)

Course Code: ECT202

Course Name: ANALOG CIRCUITS

Max. Marks: 100

Duration: 3 Hours

PART A

(Answer all questions; each question carries 3 marks)

Marks

- | | | |
|----|---|---|
| 1 | Draw the circuit of an RC integrator. Give the conditions for an RC circuit to act as integrator. | 3 |
| 2 | Define Stability factor. Derive the expression for stability factor 'S'. | 3 |
| 3 | Differentiate between dc and ac load lines. | 3 |
| 4 | What is the significance of Miller effect on high frequency amplifiers? | 3 |
| 5 | Given $K=0.4\text{mA/V}^2$ and $I_{D(ON)} = 3.5\text{mA}$ with $V_{GS(ON)} = 4\text{V}$. Determine the value of V_{TH} . | 3 |
| 6 | What are the effects of cascading in gain and bandwidth of an amplifier? | 3 |
| 7 | Differentiate positive feedback and negative feedback. | 3 |
| 8 | Draw the block diagrams of current series and current shunt feedback. | 3 |
| 9 | Illustrate the principle of output current boosting circuit in a voltage regulator? | 3 |
| 10 | What do you mean by crossover distortion? How can it be eliminated? | 3 |

PART B

(Answer one full question from each module, each question carries 14 marks)


Module -1

Given an input wave, $V_{in}=10\sin\omega t$. Setup and explain a clamper that clamps

- | | | |
|----|--|---|
| 11 | a) the wave to 22.3V at the positive peak, assuming a voltage drop of 0.7 V across the diode. Draw the output waveform and transfer characteristics also. | 8 |
| | b) Design a fixed bias circuit for a CE amplifier such that operating point is $V_{CE} = 8\text{V}$ and $I_C = 2\text{mA}$. Given, a fixed 15V d.c. supply and a silicon transistor with $\beta = 100$. Take base-emitter voltage $V_{BE} = 0.6\text{V}$ and neglect R_E . | 6 |
| 12 | a) With necessary diagrams, explain any two biasing methods of BJT. | 8 |
| | b) Set up and explain a slicer circuit that clips an input sine wave at +2V and +4V. Draw the transfer characteristics. | 6 |


Module -2

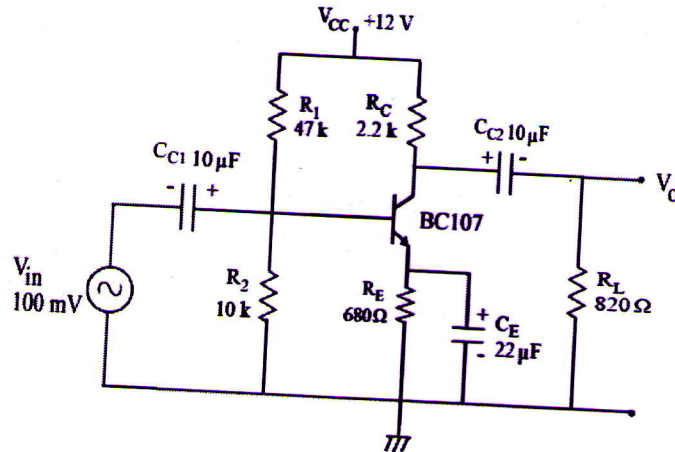- 13 a) Analyse the high frequency response of an amplifier in CE configuration using hybrid π model. 8
- b) Draw and explain the frequency response of RC coupled amplifier. 6
- Using hybrid π model, calculate the small signal voltage gain, input impedance and output impedance of the given circuit.
- Given, $V_{BE}=0.7V$, $V_A=80V$, $I_c = 2mA$ and $\beta=100$. (Neglecting r_0)



Module -3

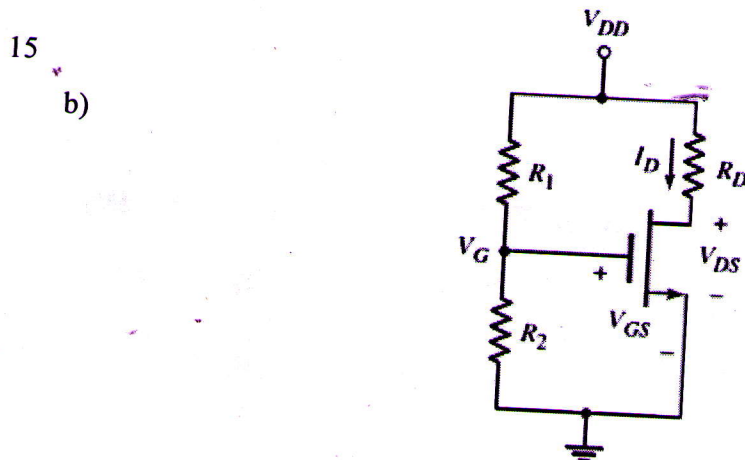- 14 a) Draw the CS stage with diode connected load and deduce the expression for voltage gain of the amplifier. 8
- Calculate the drain current and drain-to-source voltage of a common source circuit with an n-channel enhancement mode MOSFET. Find the power dissipated in the transistor.
- $R_1=22K\Omega$, $R_2=10K\Omega$, $R_D=6.8K\Omega$, $V_{DD}=8V$, $V_T=1V$, $K_n=0.1mA/V^2$



- 16 Draw the circuit of a common source amplifier using MOSFET. Derive the
a) expressions for voltage gain, input resistance and output resistance from small 8
signal equivalent circuit.
b) Briefly explain a Cascode amplifier. 6

Module -4

- 17 With neat circuit diagram, explain the discrete BJT circuit in voltage-series
feedback and derive the expression for voltage gain, input impedance and 14
output impedance.
18 a) Design wein-bridge oscillator using BJT to generate 1KHz sine wave. 9
b) With neat circuit diagram, explain the working of Hartley oscillator 5

Module -5

- 19 What are the factors affecting the variation in output voltage of voltage
regulator? With a circuit diagram, explain how load and line regulations are 14
achieved in a shunt voltage regulator.
20 Explain the working of Class B push-pull power amplifier with a neat circuit
diagram and output waveforms. Derive the expression for collector efficiency. 14
