

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

08000CS207122002  
APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree (S,FE) Examination December 2022 (2015 scheme)



Course Code: CS207

Course Name: Electronic Devices & Circuits

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer all questions, each carries 3 marks.*

Marks

- |   |   |     |
|---|---|-----|
| 1 | Draw and explain output characteristics of FET                  | (3) |
| 2 | Implement this Equation using electronic components, $Y =  2X $ | (3) |
| 3 | Write a short notes on Biased clamper with suitable waveform    | (3) |
| 4 | Draw and explain current limiting protection in IC723           | (3) |

**PART B**

*Answer any two full questions, each carries 9 marks.*

- |   |  |     |
|---|--|-----|
| 5 | a) Explain in details about voltage multipliers                                  | (6) |
|   | b) Compare BJT and FET   | (3) |
| 6 | Explain in detail how IC 723 act as low and high voltage regulators              | (9) |
| 7 | a) Draw the structure of E-MOSFET and explain with operation and characteristics | (7) |
|   | b) Prove the relation connecting $\mu$ , $g_m$ and $r_d$                         | (2) |

**PART C**

*Answer all questions, each carries 3 marks.*


- |    |  |     |
|----|--|-----|
| 8  | State and explain Barkhausen Criterion   | (3) |
| 9  | Explain about the effect of negative feedback on Bandwidth   | (3) |
| 10 | Write short notes on operating point and Load lines  | (3) |
| 11 | A 1 Pf capacitor is available, choose the inductor values in a Hartley oscillator so that $f=1\text{MHz}$ and feedback fraction is 0.2 | (3) |

**PART D**

*Answer any two full questions, each carries 9 marks.*

- |    |   |     |
|----|---|-----|
| 12 | Draw and explain the working principle of RC coupled amplifier, and sketch its frequency response | (9) |
|----|---|-----|

- 13 a) Draw and explain the working principle of Monostable multivibrator, and sketch its output waveform (7)
- b) In the Astable multivibrator,  $R_1=R_2=10K$  and  $C_1=C_2=0.01 \mu F$ . Determine the time period and frequency of the square wave. (2)
- 14 Figure shows that a silicon transistor with  $\beta=100$  is biased by base resistor method, draw the dc load line and determine the operating point. ? what is the stability factor ? (9)

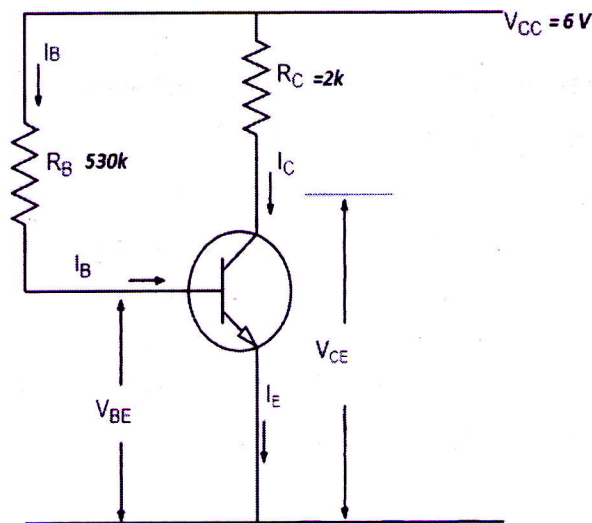


### PART E

*Answer any four full questions, each carries 10 marks.*

- 15 a) Draw and explain the working of Non-Inverting type summing amplifier using Op-amp with relevant equations (7)
- b) Discuss the two applications of summing amplifier (3)
- 16 a) Derive the expression for the voltage gain of inverting amplifier (5)
- b) Discuss the operation of an OP-amp Integrator (5)
- 17 a) For the integrator circuit shown in figure, how long does it take for the output to reach saturation? (6)

08000CS207122002

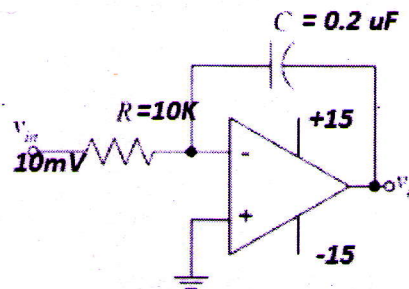

- b) Write short notes on slewrate, CMRR, input offset voltage ,offset current (4)
- 18 Using 555 IC explain the operation of astable multivibrator, with suitable waveform and sketch its internal diagram? (10)
- 19 Explain the working principle of successive approximation type ADC (10)
- 20 a) Design a first order high pass filter using opamp with cutoff frequency 2KHz and pass band gain 2. (5)
- b) Compare active and passive filter (5)

\*\*\*\*