

D

08000EC209122002



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Third Semester B.Tech Degree (S,FE) Examination December 2022 (2015 scheme)

Course Code: EC209

Course Name: ANALOG ELECTRONICS (MC)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks.

Marks

- | | | |
|---|---|-----|
| 1 | Elucidate piecewise linear model of a diode. | (5) |
| 2 | Define an expression to obtain stability factor of BJT. | (5) |
| 3 | Explain any one of feedback topologies with a diagram | |
| 4 | Give note on harmonic distortion in power amplifiers. | (5) |
| 5 | Classify oscillators with suitable examples. | (5) |
| 6 | Explain working of astable multivibrator using 555 timer IC | (5) |
| 7 | Describe offline UPS with a diagram. | (5) |
| 8 | Derive an equation for frequency of oscillation of Colpitts oscillator. | (5) |

PART B

Answer any three questions, each carries 10 marks.

- | | | |
|----|---|-----|
| 9 | a) Explain the working of any one of the clamping circuits with diagrams. | (5) |
| | b) Derive ripple factor of half wave rectifier. | (5) |
| 10 | a) Write a short note on frequency response of amplifiers. | (5) |
| | b) With diagrams, mention steps to obtain an AC equivalent circuit. | (5) |
| 11 | a) Describe the construction of FET with a diagram. | (5) |
| | b) Explain the concept of negative feedback. | (5) |
| 12 | a) Elucidate cascode amplifiers | (5) |
| | b) Derive the efficiency of class A amplifiers. | (5) |
| 13 | a) Explain the role of capacitors in amplifiers | (5) |
| | b) Write a short note on any two rectifier filters with diagrams. | (5) |

PART C

Answer any two questions, each carries 15 marks.

- | | | |
|----|---|-----|
| 14 | a) Discuss the working of bistable multivibrator using transistors. | (9) |
| | b) Give note on VCO. | (6) |
| 15 | a) Discuss in detail about lock in range and capture range. | (5) |

- b) Explain working of monostable multivibrator using 555 timer IC. (5)
- c) Derive the equation of frequency of oscillation of Hartley oscillator. (5)
- 16 a) Explain the principle of PLL in detail. (5)
- b) Illustrate the construction and characteristics of UJT. (10)
- 17 Explain RC phase shift oscillator using BJT and derive the frequency of operation (15)
