

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

Fifth Semester B.Tech (Hons.) Degree Examination December 2022 (2020 Admn.)

**Course Code: ECT 393****Course Name: FPGA BASED SYSTEM DESIGN**

Max. Marks: 100

Duration: 3 Hours

**PART A***(Answer all questions; each question carries 3 marks)*

		Marks
1	What is Behavioural Modelling in Verilog?	3
2	What is State Machine Design?	3
3	What are the limitations of FPGA?	3
4	What is a Complex Programmable Logic Device?	3
5	What is meant by configurable logic block?	3
6	Compare coarse and fine grained FPGA architecture.	3
7	What is placement and routing in FPGA?	3
8	What are the benefits of FPGAs in DSP design?	3
9	List different commercially available FPGAs.	3
10	Differentiate combinational circuit with sequential circuit.	3

**PART B***(Answer one full question from each module, each question carries 14 marks)***Module -1**

- 11 a) Write the Verilog code for a 4:1 multiplexer using behavioural model. Also write truth table and draw schematic. 8
- b) Write the test bench for 4:1 multiplexer using Verilog. 6
- 12 a) Design Verilog code for J-K Flip Flop using behavioural model. Also write truth table and draw schematic. 8
- b) Explain behavioral modelling with an example. 6

**Module -2**

- 13 a) Draw the structure of PLA and explain it. 5
- b) Implement the following Boolean expressions using a suitable PLA. 9
- A  $(x,y,z) = \sum m (1,2,4,6)$ .      B  $(x,y,z) = \sum m (0,1,6,7)$ .
- C  $(x,y,z) = \sum m (2,6)$ .      D  $(x,y,z) = \sum m (1,2,3,5,7)$ .

- 14 a) Comparison between PROM, PLA and PAL 6  
 b) Implement the following Boolean function using PAL. 8

$$F_1(A,B,C) = (1, 2, 4, 5, 7). F_2(A,B,C) = (0, 1, 3, 5, 7)$$

**Module -3**


- 15 a) With neat diagram explain the internal architecture of FPGA. 14  
 16 a) Explain Logic block with neat diagram. 7  
 b) Draw and explain I/O block architecture of FPGA. 7

**Module -4**

- 17 a) Explain in detail three major classes of placement in FPGA. 10  
 b) Explain the placement issues in FPGA. 4  
 18 a) With neat diagram explain different Programmable interconnections in FPGA 8  
 b) Explain FPGA Routing Techniques. 6

 **Module -5**

- 19 a) What is LUTs in FPGA? Design and implement the following combinational circuit using LUTs in FPGA. 7



- b) Explain with diagram, how to implement an 8 bit adder using 8 bit LUTs and 4 bit LUTs. 7  
 20 a) With neat diagram explain the architecture of Xilinx Virtex. 14

\*\*\*