

D

1200ECT322052301

Pages: 2

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Sixth Semester B.Tech Degree Supplementary Examination May 2023 (2019 Scheme)



Course Code: ECT322

Course Name: POWER ELECTRONICS

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 3 marks.

		Marks
1	Compare power BJT, MOSFET and IGBT for switching applications.	(3)
2	Draw the switching characteristics of power BJT.	(3)
3	List the advantages of 3 phase rectifier over single phase.	(3)
4	What is a snubber circuit?	(3)
5	For a Buck Converter, $R = 1\Omega$, $V_i = 40V$, $V_o = 5V$. Find the duty ratio.	(3)
6	Draw the circuit of half bridge converter.	(3)
7	What is space vector modulation?	(3)
8	Define inverter. Also list its classification based on the strategy used for driving power semiconductor switches.	(3)
9	What is four quadrant operation of dc drive?	(3)
10	List the advantages of induction motor.	(3)

PART B

Answer one full question from each module, each carries 14 marks.

Module I

- 11 a) With neat waveforms, explain the static and dynamic characteristics of the power diode. (7)
- b) Draw the structure of the power transistor and explain its operation with its transfer characteristics. (7)

OR

- 12 a) With structure, describe the working of IGBT. (8)
- b) Illustrate the methods used to turn on and turn off GTO. (6)

Module II

- 13 a) Illustrate any two MOSFET drive circuits. (6)

- b) Explain the working of shunt snubber with relevant circuit diagram, waveform. (8)
Also deduce the equation for resistor and capacitor value. .

OR

- 14 a) Derive the expression of average output voltage of single-phase full wave- (6)
controlled rectifier with R load along with neat diagram and waveform.
b) Explain the working of three-phase diode bridge rectifier. (8)

Module III

- 15 a) Draw and explain the circuit diagram of the Boost converter with switching (10)
waveform.
b) Define buck-boost converter. When it will act as a buck converter and boost (4)
converter?

OR

- 16 a) Discuss full-bridge converter with circuit diagram and waveforms. (7)
b) Explain the working of push-pull converters with circuit diagram. (7)

Module IV

- 17 Illustrate the different modes of operation of full bridge inverter with RL Load. (14)

OR

- 18 Enumerate the working principle of three phase inverter. (14)

Module V

- 19 a) Explain the working principle of induction motor. (10)
b) Why rotor never runs at synchronous speed? (4)

OR

- 20 a) Mention two industrial applications of power electronics. (7)
b) Mention two residential applications of power electronics. (7)
