

B

03000EC304052004

Pages: 2

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S6 (S,FE) / S4 (PT) (S,FE) Examination May 2023 (2015 Scheme)



Course Code: EC304

Course Name: VLSI

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer any two full questions, each carries 15 marks*

Marks

- 1 a) Explain any two methods of fabricating resistors in Integrated Circuits? (8)
- b) Distinguish between dry and wet etching? (7)
- 2 a) Discuss the role of Vapour Phase Epitaxy (VPE) in IC fabrication. With schematic diagram, explain any two VPE techniques. (9)
- b) Distinguish between Czochralski and Float Zone process of Silicon crystal growth. (6)
- 3 a) Derive Deal Grove Model for thermal oxidation? (10)
- b) Discuss the significance of Linear Rate and Parabolic rate coefficients. (5)

**PART B**

*Answer any two full questions, each carries 15 marks*

- 4 a) Draw the Voltage Transfer characteristics of CMOS inverter. Explain its DC characteristics (9)
- b) Implement  $4 \times 1$  multiplexer using complementary pass transistor logic (6)
- 5 a) "Transmission gate logic can transmit strong zeros and strong ones." Justify the statement (6)
- b) Draw the circuit diagram, stick diagram and layout diagram of a 3 input CMOS NOR Gate. (9)
- 6 a) List  $2\mu\text{m}$  design rules for CMOS Technology? (8)
- b) What are the various types of power dissipation in CMOS inverters? Derive an expression for the total power dissipation. (7)

**PART C**

*Answer any two full questions, each carries 20 marks*

- 7 a) With the help of suitable diagram, explain the working of NOR based ROM. (10)
- b) With suitable block diagrams, explain the internal architecture of Xilinx 4000 FPGA configurable logic block. (10)
- 8 a) Draw the block diagrams of carry ripple adder and carry-by pass adder. List the limitations of carry ripple adders. How carry-by pass adder overcomes the limitation of carry ripple adder. (10)
- b) Draw the circuit diagram of a 6T CMOS SRAM cell. With suitable circuit diagram, explain the read and write operations in 6T CMOS SRAM cell. (10)
- 9 a) Draw the circuit diagram of a one-transistor DRAM cell. Explain the read and write operation in one-transistor DRAM cells (10)
- b) With block diagrams, distinguish between linear carry select adder and square root carry select adder. (10)

\*\*\*\*