

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Fourth Semester B.Tech (Honours) Degree Examination June 2023 (2021 Admission)


**Course Code: EET292****Course Name: NETWORK ANALYSIS AND SYNTHESIS**

Max. Marks: 100

Duration: 3 Hours

PART A*(Answer all questions; each question carries 3 marks)*


- | | | Marks |
|---|--|-------|
| 1 | Describe the following terms a) Tree b) Co-Tree c) Twig d) link e) Cut-set f) Tie-set | 3 |
| 2 | For the given circuit draw the graph, one tree and its co-tree | 3 |

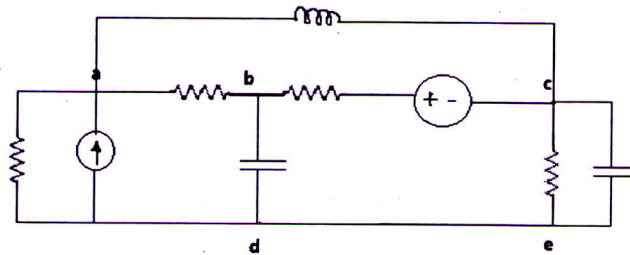

- | | | |
|----|---|---|
| 3 | Explain the concept of duality with the help of a suitable example | 3 |
| 4 | State Tellegen's theorem. write two applications | 3 |
| 5 | Derive image impedance of an LTI two port network in terms of ABCD parameters | 3 |
| 6 | Draw the ideal response of (a) Low pass filter (b) high pass filter filter (c) Band Pass filter (d) Band stop filters | 3 |
| 7 | Write the properties of positive real function | 3 |
| 8 | Write the necessary and sufficient condition for positive real function | 3 |
| 9 | Draw the Foster and Cauer Form of LC networks | 3 |
| 10 | How can a circuit is realized from the network function using Cauer Form. | 3 |

PART B*(Answer one full question from each module, each question carries 14 marks)***Module -1**


- | | | |
|----|--|----|
| 11 | a) For the network shown draw the oriented graph, also write the node equation | 10 |
|----|--|----|

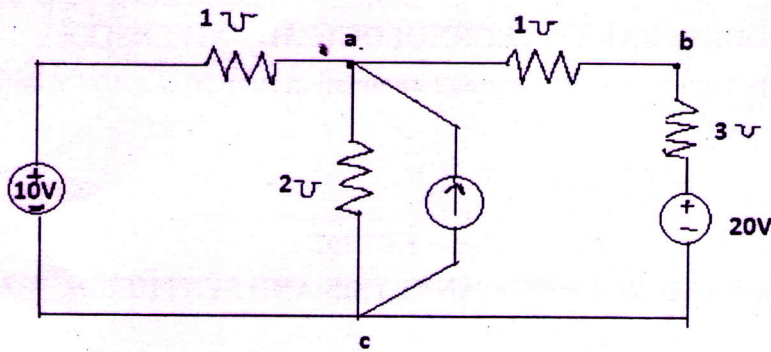

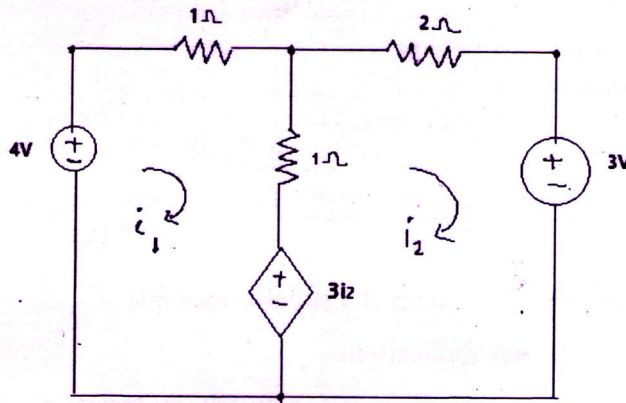- b) A reduced Incident matrix of a graph is given by
$$\begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix} \quad 4$$


Obtain the number of possible trees

- 12 a) For the network given using loop method of analysis, determine the currents in all the branches, indicating their direction 14




Module -2

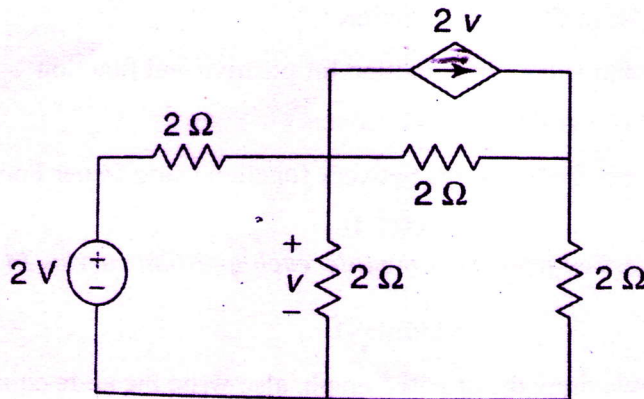- 13 a) For the network shown obtain the equilibrium equation on node basis and calculate 'v' 14



- 14 a) Find the power delivered by each dependent source in the given circuit

14

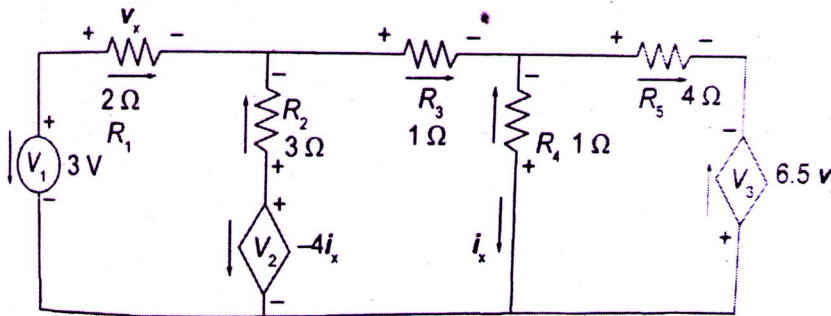


Module -3


- 15 a) Derive the characteristic impedance and propagation constant of symmetric T and PI networks under sinusoidal steady state 10
- b) What is constant-K and m-derived filters 4
- 16 a) Design a low pass filter (both π and T-networks) having a cut-off frequency of 1KHz to operate with terminated load resistance of 200Ω 5
- b) Design T and π network of m-derived high pass filter having nominal 9 characteristic impedance $R_0 = 900\Omega$, cut off frequency $f_c = 2$ KHz and infinite attenuation(or resonant) frequency $f_\infty = 1.8$ KHz

Module -4

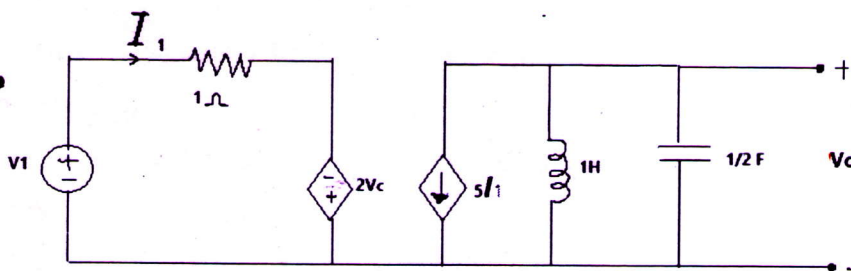- 17 a) For the network shown, draw the pole-zero plot of $\frac{V_c}{V_1}$ 9



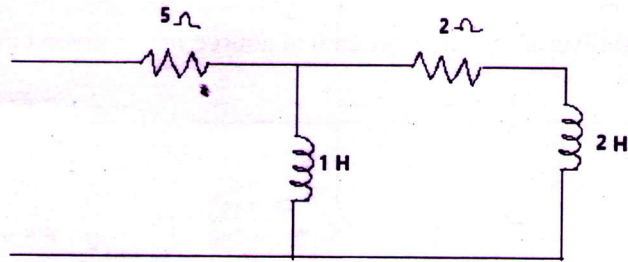- b) Determine the range of β such that the polynomial $P(s) = s^4 + s^3 + 4s^2 + \beta s + 3$ is Hurwitz 5
- 18 a) The transfer function of the network is given by $T(s) = \frac{1}{1 + sCR}$ find its impulse response. Also obtain the pole-zero plot in the s- plane of the driving point impedance function for the network shown. 7



- b) Verify the given function is positive real function

7

$$F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$$

Module -5

- 19 a) An impedance function is given by

10

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

find the R-C representation of Foster I and II forms

- b) Synthesize $Z(s) = \frac{(s+1)(s+3)}{s(s+2)}$ in Cauer's I form

4

- 20 a) If $Z(s) = \frac{(s+4)(s+6)}{(s+3)(s+5)}$ find Cauer- I and II form

10

- b) What are the properties of R-C impedance or R-L admittance functions

4
