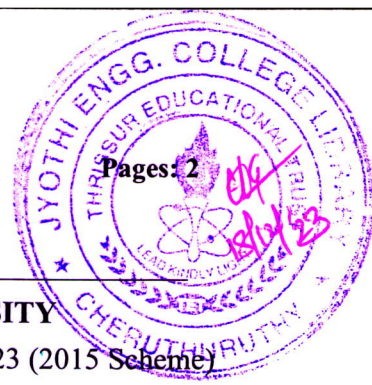


C

08000EE203122002



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (S, FE) / S1 (PT) (S, FE) Examination December 2023 (2015 Scheme)

Course Code: EE203

Course Name: ANALOG ELECTRONICS CIRCUITS

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks.

Marks

1. Design a clamper circuit to clamp a $10V_{pp}$ sine wave so that its positive peak is clamped at +3V. Assume diode drop is 0.7V. Draw and explain the output waveform and transfer characteristics. (5)
2. Explain the construction and working of n-channel JFET. (5)
3. What are the four topologies of a feedback amplifier? Identify input signal, output signal, feedback signal and transfer gains of each topology. (5)
4. Design a RC phase shift oscillator using transistor for generating a 2 kHz sinusoidal signal. (5)
5. Explain the working of a Half Wave Precision Rectifier specifying the role of op-amp. (5)
6. Derive the expression for voltage gain for an inverting amplifier. (5)
7. Draw the circuit diagram of a triangular wave generator. Sketch the waveforms and explain the circuit operation. (5)
8. Explain the working of a Wein bridge oscillator using op-amp. (5)

PART B

Answer any two full questions, each carries 10 marks.

- 9 a) Design a collector to base bias circuit to have an operating point of $V_{CE}=6V$ and $I_C=5mA$. The supply voltage is 15V and transistor h_{FE} is 125 (5)
- b) Explain the operation of n-channel depletion type MOSFET, with the help of its drain and transfer characteristics. (5)
- 10 a) Draw the hybrid equivalent model of common emitter amplifier and derive the expression for current gain and voltage gain. (5)
- b) Draw the small signal equivalent diagram of Common Drain FET amplifier and derive the expression for output impedance and voltage gain. (5)

- 11 a) Explain the bias compensation method using thermistor. (5)
b) Explain the working of FET as a switch and voltage-controlled resistor. (5)

PART C

Answer any two full questions, each carries 10 marks.

- 12 a) Explain the working of Class A Power amplifier and derive its maximum power conversion efficiency. (5)
b) Derive the expression for frequency of a Wein Bridge Oscillator using transistor. (5)
- 13 a) What is cross over distortion in power amplifier and how this is eliminated. (5)
b) With a neat diagram explain the working of a fundamental differential amplifier. (5)
- 14 a) Draw the circuit diagram of a transformer coupled amplifier and explain its working. (5)
b) With a neat diagram explain the working of a Hartley oscillator. (5)

PART D

Answer any two full questions, each carries 10 marks.

- 15 a) Draw the circuit diagram of an op-amp inverting Schmitt Trigger circuit. Sketch typical input output waveform and explain circuit operation. Write equation for the upper and lower triggering point. (5)
b) Design a square wave generator using 555 timer to produce an output signal of 2kHz frequency having 25% duty cycle. (5)
- 16 a) Explain the working of differentiator circuit using op-amp. (5)
b) With neat circuit diagram explain the working of RC phase shift oscillator using op-amp. Mention its disadvantages. (5)
- 17 a) Explain the working of an astable multivibrator using 555 IC with its internal diagram. (5)
b) With a neat diagram explain the working of an instrumentation amplifier. Mention its application. (5)
