

B

08000EE201122005



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (S, FE) / S3 (PT) (S, FE) Examination December 2023 (2015 Scheme)

Course Code: EE201

Course Name: CIRCUITS AND NETWORKS

Max. Marks: 100


Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks.

Marks

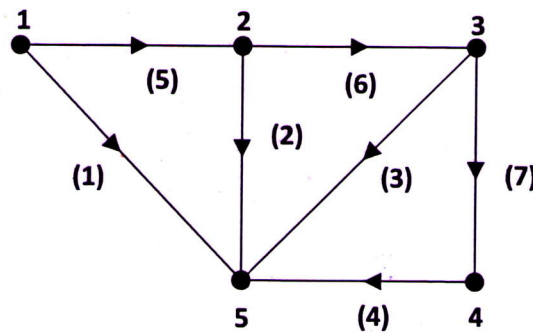- 1 State and prove maximum power transfer theorem for DC circuits (5)
- 2 Find the tie-set matrix for the network graph given below and express branch currents in terms of loop currents. Select {1,4,6} as links. (5)



- 3 A series RLC circuit has $L = 1H$ and $C = 1F$ and $R = 10\Omega$. Find the expression for the current if the capacitor has an initial voltage of 10V and is discharged through the resistor and inductor. (5)

- 4 The current through a 2F capacitor is given by the following s-domain equation. (5)

$$I(s) = \frac{2s + 4}{s^2 + 4s + 3}$$

Determine the voltage across the capacitor, $v(t)$.

- 5 Derive the conditions of symmetry and reciprocity of a two port network in terms of transmission parameters. (5)

- 6 A two port network 'A' has $[Z]_A = \begin{bmatrix} 2 & 1 \\ 1 & 3 \end{bmatrix}$ and another two port network 'B' (5)


has $[Y]_B = \begin{bmatrix} 1 & -1 \\ -2 & 3 \end{bmatrix}$. If the two networks A and B are connected in series, find the Z parameters of the overall network.

- 7 Test whether the polynomial $s^4 + 2s^3 + 6s^2 + 3s + 4$ is Hurwitz or not. (5)
- 8 List any five properties of RC driving point impedance functions. (5)

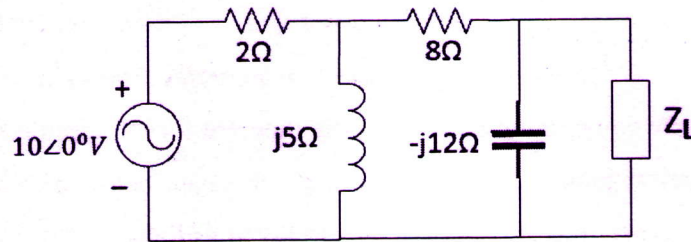
PART B

Answer any two full questions, each carries 10 marks.

- 9 In the circuit given below, determine the value of the load impedance Z_L , for maximum power transferred by the source to the load. Also, compute the maximum power transferred. (10)



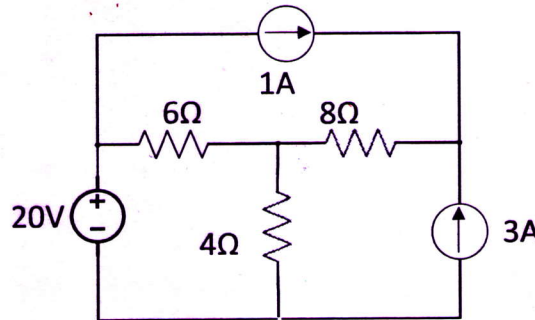
- 10 a) For the circuit shown below, determine the current through the 4Ω resistor using Norton's theorem. (5)



- b) The incidence matrix of a graph is given below. Draw the oriented graph. (5)

Nodes ↓	Branches →						
	1	2	3	4	5	6	7
1	1	0	0	0	1	0	0
2	0	1	0	0	-1	1	0
3	0	0	1	0	0	-1	1
4	0	0	0	1	0	0	-1

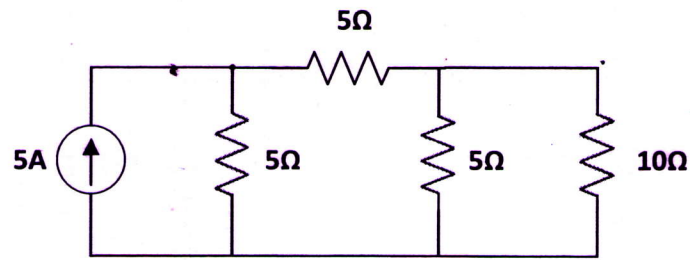
- 11 Obtain the oriented graph of the following circuit and determine the voltage across the 10Ω resistor using the network equilibrium equations based on KCL. (10)




PART C

Answer any two full questions, each carries 10 marks.

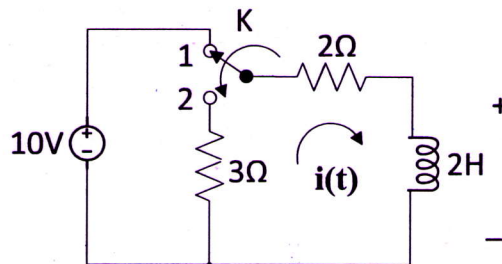
12. In the circuit shown below, the switch was initially at position 1 and the steady state condition is reached. At $t = 0$, the switch is changed to position 2. Determine (i) voltage across the inductor immediately after the switching operation (ii) expression for the current $i(t)$ for $t > 0$ and (iii) expression for the voltage across the inductor for $t > 0$. (10)



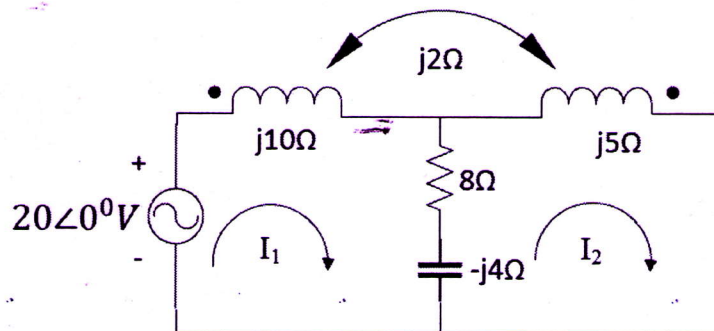- 13 a) A resistor R and a $1F$ capacitor is connected in series with a $50V$ DC supply. (5)
Determine the value of the resistance R if the voltage across the capacitor reaches 50% of its steady state value in 5 seconds.
- b) Determine the current I_2 in the following circuit. (5)



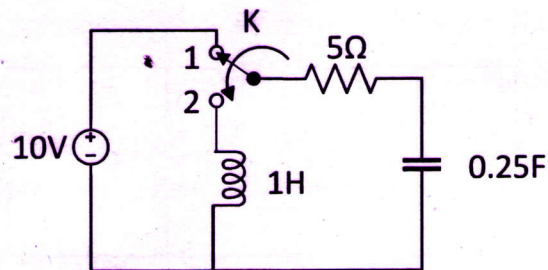
- 14 The switch K in the following circuit has been at position 1 for a long time and the steady state condition is reached. At $t = 0$, the switch is moved to position 2. Using Laplace transform, find an expression for the current through the resistor for $t > 0$. (10)



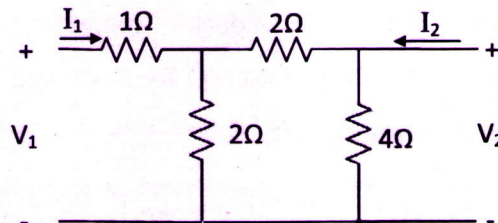PART D

Answer any two full questions, each carries 10 marks.

- 15 a) Find the z parameters of the following network and hence determine whether the network is reciprocal. (5)



- b) Find the equivalent T network of a two port network represented by the following equations. (5)

$$V_1 = 2I_1 + I_2$$

$$V_2 = I_1 + 3I_2$$

- 16 a) Express hybrid parameters in terms of Y parameters. (5)
- b) Test whether the following function is a positive real function. (5)

$$Z(s) = \frac{s(s+3)(s+5)}{(s+1)(s+4)}$$

- 17 Obtain the Foster I and II forms of the following impedance function (10)

$$Z(s) = \frac{s(s+4)(s+6)}{(s+1)(s+5)}$$
