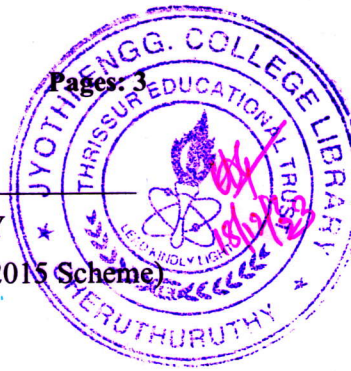


B

08000EC201122001



Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (S, FE) / S1 (PT) (S, FE) Examination December 2023 (2015 Scheme)

Course Code: EC201

Course Name: NETWORK THEORY

Max. Marks: 100


Duration: 3 Hours

PART A


Answer any two full questions, each carries 15 marks.

Marks

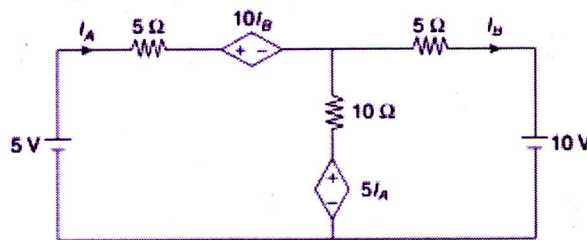- 1. a) List the classifications of dependent and independent sources. (7)
- b) Find the currents I_A and I_B in the network using Mesh analysis. (8)



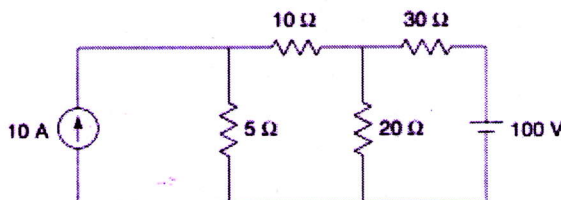- 2. a) Find the current through 10 ohm resistor using node analysis. (7)



- b) State and prove time shifting theorem in Laplace transform. (8)
- 3. a) Find the Laplace transform of $t \cos^2 t$. (8)
- b) State and Prove maximum Power transfer theorem. Derive the expression for maximum power P_{max} (7)

PART B

Answer any two full questions, each carries 15 marks.

- 4. a) Solve $y'' + 4y = \delta(t)$, $y(0) = 0$, $y'(0) = 0$ Using Laplace transform. (8)

- b) Find the Inverse Laplace transform of the following function. (7)


$$I(s) = \frac{8}{(s+3)(s+5)}$$

5. a) How to determine the time domain behaviour of a system from the pole-zero plot? (7)
 b) Find the step and impulse response of series R-L circuit. (8)
6. a) Draw the pole - zero plot for the function $F(s) = \frac{s(s+2)}{(s+3)(s+1)^2}$ (5)
 b) What are the restrictions on pole and zero locations for driving point and transfer functions? (10)


PART C

Answer any two full questions, each carries 20 marks.

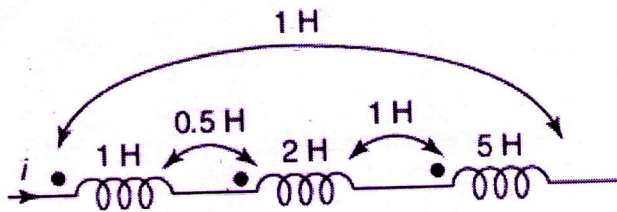7. a) Express Z parameters in terms of ABCD parameters. (8)
 b) Find the equivalent inductance of the following network. (4)



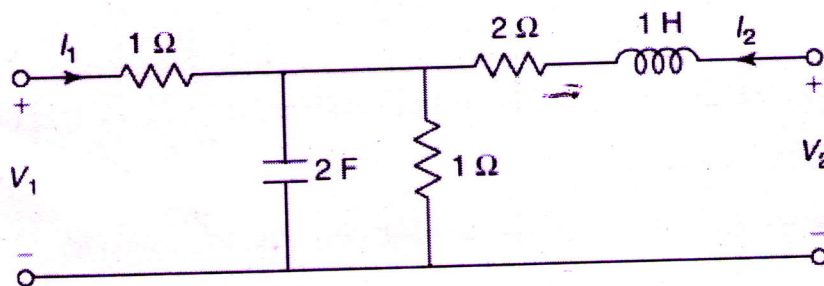- c) Find the Z - parameter of the following network. (8)



8. a) Two two port networks are connected in cascade. Let the transmission matrices

of the networks are $\begin{bmatrix} A1 & B1 \\ C1 & D1 \end{bmatrix}$ and $\begin{bmatrix} A2 & B2 \\ C2 & D2 \end{bmatrix}$ respectively. Form the

transmission parameter representation and inverse transmission parameter representation of the cascaded network. (14)

b) Explain about the following terms i) Characteristic impedance, ii) Q factor iii) Propagation constant. iv) Selectivity (6)

9. a) Compare series and parallel resonance circuits. (7)

b) Derive the expression for Quality factor of a series resonant circuit. (6)

c) A series resonant circuit has the parameter values $R = 100 \text{ ohm}$, $L = 0.01\text{H}$
 $C = 100 \mu\text{F}$. Calculate its i) resonant frequency and ii) Band width. (7)
