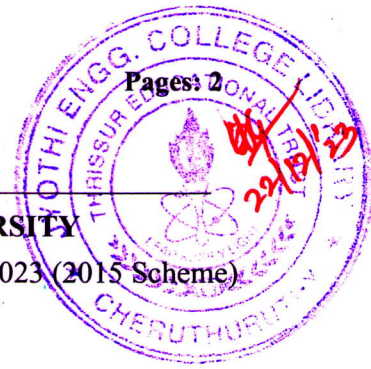


Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (S, FE) / S1 (PT) (S, FE) Examination December 2023 (2015 Scheme)



Course Code: CS207

Course Name: Electronic Devices & Circuits


Max. Marks: 100

Duration: 3 Hours

PART A*Answer all questions, each carries 3 marks.*

Marks

- | | | |
|---|--|-----|
| 1 | Draw a differentiator circuit and draw the input and output waveforms for Square wave input. | (3) |
| 2 | Verify whether the following circuit will work as a clamper | (3) |

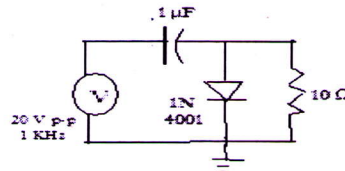

- | | | |
|---|--|-----|
| 3 | Draw and explain the circuit of a 78XX IC based voltage regulator. | (3) |
| 4 | Draw and explain output characteristics of FET | (3) |

PART B*Answer any two full questions, each carries 9 marks.*

- | | | |
|---|--|-----|
| 5 | a) Compare series and shunt voltage regulators. | (3) |
| | b) Draw the characteristics and explain the working of an n-channel JFET. | (6) |
| 6 | a) Draw and explain the circuit of a slicer for levels of -3V and -6V. | (4) |
| | b) Draw and explain the block diagram of SMPS. | (5) |
| 7 | a) Draw the circuit of a transistor shunt regulator and explain its working. | (5) |
| | b) Assuming suitable values, design an integrator circuit for a 1 KHz square wave. Draw the relevant waveforms and circuit with designed components. | (4) |

PART C*Answer all questions, each carries 3 marks.*

- | | | |
|----|--|-----|
| 8 | Compare positive feedback with negative feedback. | (3) |
| 9 | Explain the effect of cascading on amplifier's gain and bandwidth. | (3) |
| 10 | What is mean by operating point of a transistor? | (3) |
| 11 | Draw the circuit diagram for bistable multivibrator and give a simple explanation? | (3) |

PART D

Answer any two full questions, each carries 9 marks.

- 12 a) Draw the circuit diagram and explain the working of a common source MOSFET amplifier. (4)
b) Draw the circuit diagram and explain the working of Wien bridge oscillator for an output frequency of 6 KHz. (5)
- 13 a) With neat diagram explain the working of Hartley oscillator using BJT. (4)
b) Derive the expression for frequency of oscillation and loop gain of a Hartley oscillator using BJT (5)
- 14 With circuit diagram and design equations explain the working of a monostable multivibrator (9)

PART E

Answer any four full questions, each carries 10 marks.

- 15 a) Define: (1) Slew rate, (2) CMRR, (3) offset voltage (4) Offset current (8)
b) What are their practical values for parameters of op-amp IC 741 (2)
- 16 a) Draw the circuit diagram and frequency response of a second order high pass Butterworth filter using OP-AMP and explain its working. (5)
b) Design a first order Butterworth LPF using OP-AMP for a high cut of frequency of 1KHz and pass band gain is 2. Give the design steps and draw the frequency response. (Assume $C=0.01\mu\text{F}$) (5)
- 17 Using 555 timer, Explain the operation of monostable multivibrator with necessary waveforms. (10)
- 18 a) Draw the circuit diagram of a 3-input summing amplifier using Op-Amp and explain its working with supporting derivations. (5)
b) Sketch the circuit of an integrator circuit using Op-Amp and prove that the integration happens on the input signal. (5)
- 19 a) Explain the concept of Binary weighted resistor DAC. What are its drawbacks? In a 10 bit DAC, Reference voltage is given as 15v. Find analog output for digital input of 1011011001. (10)
- 20 a) With functional block diagram, explain the working of 555 Timer IC. (4)
b) Write design equations and pin out of 555 TIMER IC working as astable Multivibrator to generate a wave form of 1KHz., with 50% duty cycle. (6)
