

D

010BE10104022301


Pages: 3

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

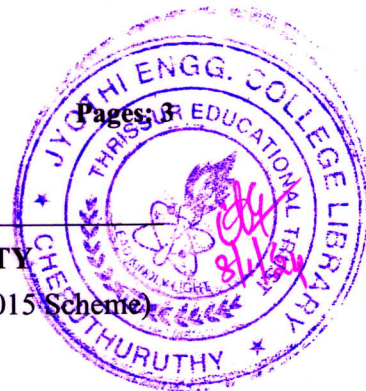B.Tech Degree S1 (S, FE) S2 (S, FE) Examination December 2023 (2015 Scheme)



Course Code: BE101-04

Course Name: INTRODUCTION TO ELECTRONICS ENGINEERING

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks

Marks

- | | | |
|---|---|-----|
| 1 | Explain the construction of carbon film resistor. | (5) |
| 2 | Explain the formation of n-type and p-type semiconductors. | (5) |
| 3 | What is the need for biasing a transistor? Give one example of transistor biasing. | (5) |
| 4 | Give the principle of operation of an SCR. | (5) |
| 5 | Design a shunt clipper circuit that limits the output voltage between +2V and -4V if a 10 V peak-to-peak sine signal is given as the input. | (5) |
| 6 | Draw the block diagram of regulated DC power supply and give the need of each stage. | (5) |
| 7 | Define resolution and accuracy of measuring instruments. | (5) |
| 8 | How is frequency of a waveform measured using CRO? | (5) |

PART B

Answer six questions, one full question from each module and carries 10 marks.

MODULE I

- | | | |
|---|---|-----|
| 9 | a) Explain the construction details of electrolytic capacitor. | (6) |
| | b) What will be the range of resistance value of a resistor with colour coding Brown, Black, Green, Gold. | (4) |

OR

- | | | |
|----|--|-----|
| 10 | a) With suitable diagrams explain the working principle of an electromechanical relay. | (6) |
| | b) Give any 4 specifications of an inductor. | (4) |

MODULE II

- | | | |
|----|---|-----|
| 11 | a) Explain the working principle of i) Solar cell ii) LED | (6) |
| | b) Write short note on the breakdown mechanisms in a diode. | (4) |

OR

- 12 a) Draw and explain the forward and reverse characteristics of a diode. (6)
 b) Explain the working of a photodiode. (4)

MODULE III

- 13 a) Explain the circuit of a common emitter RC coupled amplifier using NPN transistor. (6)
 b) Draw the frequency response of a RC coupled amplifier and explain how gain reduces at low and high frequencies. (4)

OR

- 14 a) With neat sketches, explain the input and output characteristics of a BJT in CE configuration. (6)
 b) If the base current of a transistor $I_B = 100\mu\text{A}$, determine the collector and emitter currents. Given $\beta_{dc} = 110$. (4)

MODULE IV

- 15 With neat diagrams explain the structure, characteristics and regions of operation of an n-channel enhancement MOSFET. (10)

OR


- 16 a) Explain the structure and principle of operation of JFET. (6)
 b) Compare enhancement and depletion MOSFETs. (4)

MODULE V

- 17 a) Draw and explain the circuit of a bridge rectifier with capacitive filter. (6)
 b) Derive the expression for V_{dc} of a full wave rectifier. (4)

OR

- 18 a) Explain how a Zener diode can be used as a voltage regulator. (6)
 b) What will be the output waveform of the given diode circuit if $V_m = 10\text{V}$ and $V_r = 2\text{V}$? Assume that the diode is ideal one. (4)

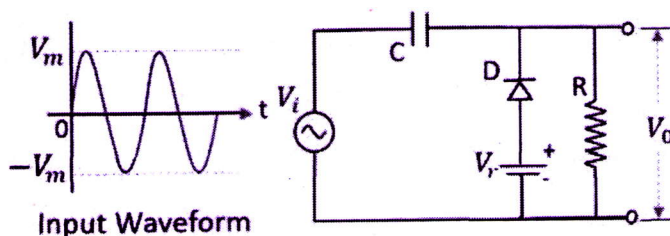

MODULE VI

- 19 a) Explain the construction of a basic CRT. (6)
b) Differentiate between absolute error and relative error in measurements. (4)

OR

- 20 a) Sketch the basic block diagram of a DSO and explain the operation. (6)
b) How do you test a transistor using multimeter? (4)
