

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

08000ECT205122302

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S3 (R, S) / S1 (PT) (S, FE) Examination December 2023 (2019 Scheme)



Course Code: ECT205

Course Name: NETWORK THEORY


Max. Marks: 100

Duration: 3 Hours


**PART A**

Answer all questions. Each question carries 3 marks

- |  | Marks |
|--|-------|
| 1 Differentiate dependent and independent sources.                       | (3)   |
| 2 Explain the concept of super-mesh with the help of a suitable example. | (3)   |
| 3 State reciprocity theorem.   | (3)   |
| 4 Find the current through 20 Ω resistor using superposition theorem.    | (3)   |

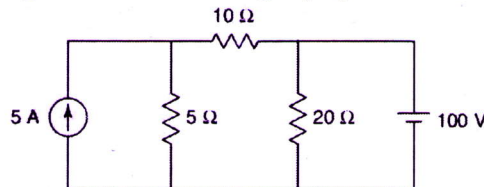

- |  |     |
|--|-----|
| 5 State the initial value theorem and find the initial value of the function, $f(t)$ which have Laplace transform, $F(s) = \frac{s^2 + 1}{s(2s+3)(s+5)}$ . | (3) |
| 6 Find the expression for the current through an RC circuit due to impulse as input.   | (3) |
| 7 State the properties of a network transfer function.   | (3) |
| 8 Find the driving point impedance function of the following network.  | (3) |

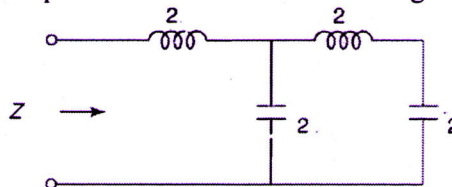


- |   |     |
|---|-----|
| 9 Derive the conditions of reciprocity in a two-port network in terms of its transmission parameters.   | (3) |
| 10 Consider a two-port network with the open circuit impedance parameter matrix $\begin{bmatrix} 2 & 1 \\ 3 & 2 \end{bmatrix}$ . Check whether the network is symmetric and reciprocal. | (3) |

**PART B**


Answer any one full question from each module. Each question carries 14 marks

**Module 1**

- |   |     |
|---|-----|
| 11 a. Using node analysis determine the voltage $V_x$ . | (8) |
|---|-----|

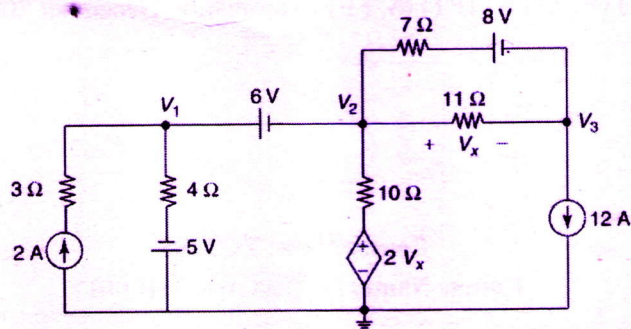

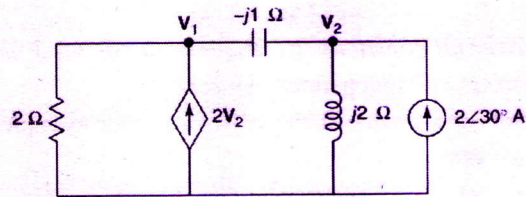
b. Find the node voltages of the following circuit.



(6)


12 a. Find the current through 10 Ω resistor using mesh analysis.

(6)

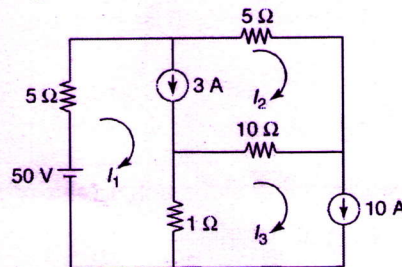

(8)


b. Find the loop current  $I_1$  and  $I_2$  in the given network.

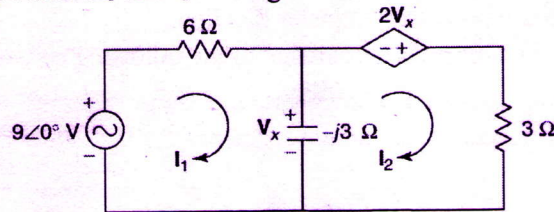

**Module 2**


13 a. Find the value of  $R_L$  such that maximum power is transferred to it. Also find the maximum power transferred to  $R_L$

(7)

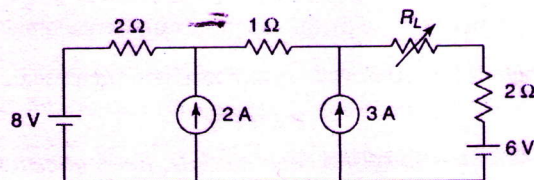


b. Find the current through  $j3 \Omega$  using superposition theorem.


(7)

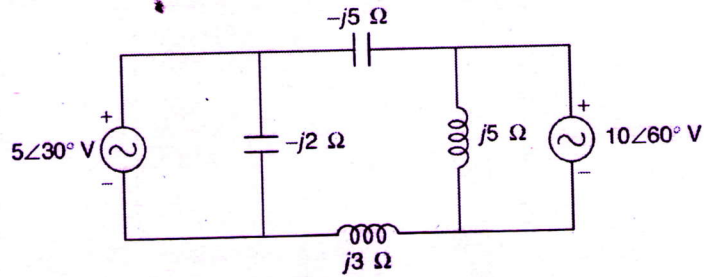

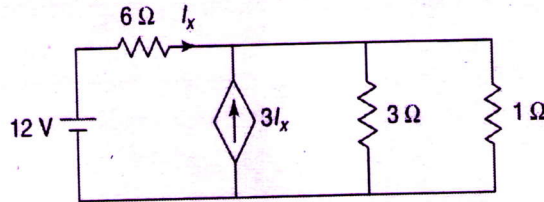- 14 a. Find the current through  $1\Omega$  resistor using Norton's method. (8)




- b. Obtain the Thevenin's equivalent of the network with respect to terminals  $AB$ . (6)

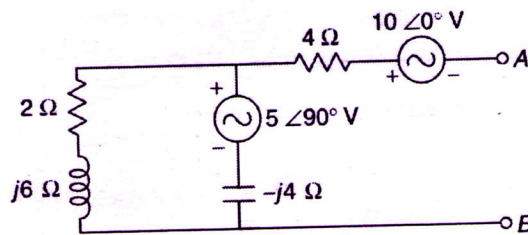

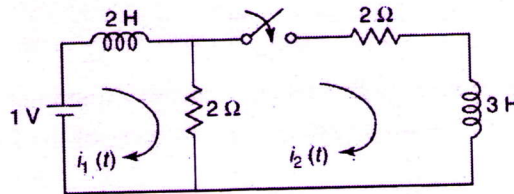**Module 3**

- 15 a. In the circuit, the switch is closed at  $t = 0$ . Determine current through the inductor with inductance  $3H$  for  $t > 0$ . Assume the steady state being reached before  $t = 0$ . (8)




- b. Find the Laplace transform of the following signals (6)


i)  $\int_0^t e^{-4t} \sin 2t$

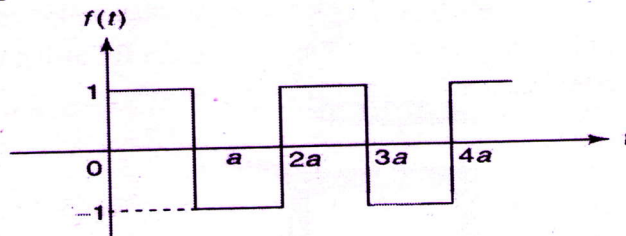ii)  $\frac{1 - e^{-t}}{t}$

- 16 a. Find the Laplace transform of the waveform  $f(t)$ . (6)




- b. In the given network, the switch is moved from position a to b at  $t = 0$ . Determine the voltage,  $V_C(t)$ . (8)

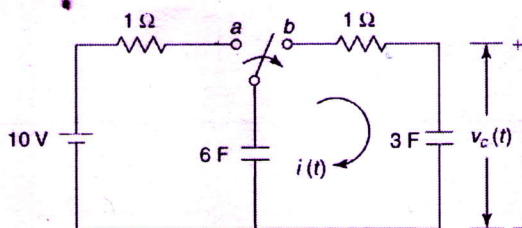

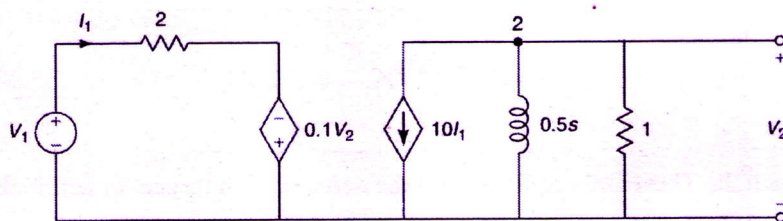
**Module 4**

- 17 a. Find the driving point admittance function,  $Y_{11} = \frac{I_1}{V_1}$  of the following network. (6)




- b. The voltage of a network is given as  $V(s) = \frac{(s+2)(s+6)}{(s+1)(s+5)}$ . Plot the pole-zero diagram and hence obtain  $V(t)$ . (8)

- 18 Find the network functions  $\frac{V_2}{I_1}$ ,  $\frac{V_2}{V_1}$  and  $\frac{V_2}{I_2}$  of the following network. (14)

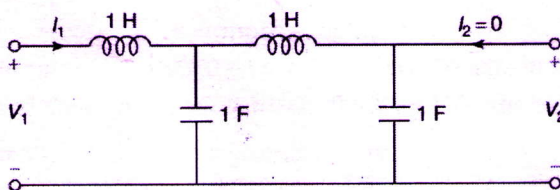


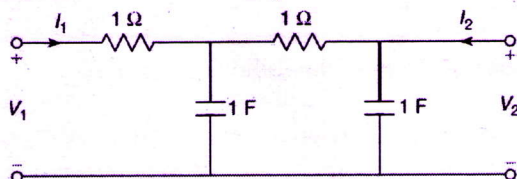**Module 5**

- 19 a. Express the transmission parameters in terms of Z-parameters and h-parameters. (7)  
 b. Determine the short circuit admittance parameters of the following network. (7)



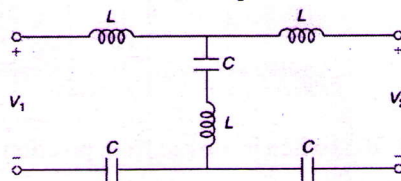- 20 a. Show that when 2 two-port networks are connected in series, the resultant Z-matrix is the sum of Z-matrices of each individual network. (6)  
 b. Find the open circuit impedance parameters of the following circuit using the concept of series interconnection of two-port networks. (8)



\*\*\*\*\*