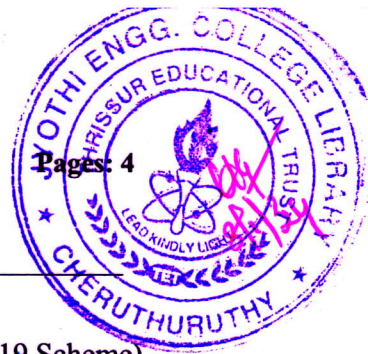


B

0800EET201122103



Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

B.Tech Degree S3 (R, S) / S1 (PT) (S, FE) Examination December 2023 (2019 Scheme)

**Course Code: EET201**

**Course Name: CIRCUITS AND NETWORKS**

Max. Marks: 100


Duration: 3 Hours

**PART A**


*Answer all questions. Each question carries 3 marks*

Marks

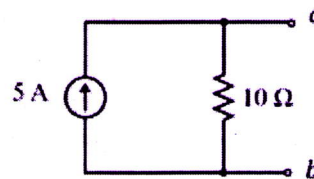- 1 State and explain Reciprocity Theorem. (3)
- 2 Find the value of the load resistance to be connected at  $a - b$  so that maximum power is transferred by the source. What is the maximum power delivered to the load? (3)



- 3 A series  $RL$  circuit with  $R = 20 \Omega$  and  $L = 10 H$  has a constant voltage  $V = 40 V$  applied through switch  $S$  at  $t = 0$ . Determine the current equation in the network. (3)
- 4 What is the time constant of a series  $RC$  circuit with  $R = 10 \Omega$  and  $C = 1 \mu F$ ? (3)
- 5 Derive the  $s$ -domain equivalent circuit of an inductor having an initial current of  $I_0$ . (3)
- 6 Obtain the equivalent inductive reactance. (3)

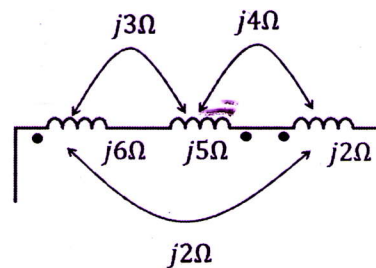

- 7 Line currents through a 3-phase 4-wire unbalanced star-connected load are  $I_A = 9.24 \angle 0^\circ A$ ,  $I_B = 21 \angle -100^\circ A$  and  $I_C = 15.4 \angle 110^\circ A$ . Find the current through the neutral wire. (3)
- 8 For a series RLC circuit show the variation of impedances with frequency graphically. (3)

- 9 Two identical sections of transmission line with  $A = 2, B = 3, C = 1, D = 2$  parameters are cascaded. Calculate the transmission parameters of the resultant network. (3)


- 10 A two-port network is described by the equation, (3)
- $$V_1 = 4I_1 + 2I_2 \text{ and } V_2 = 2I_1 + I_2.$$
- A load impedance of  $3\Omega$  is connected at port 2. Calculate the value of input impedance.

**PART B**


*Answer any one full question from each module. Each question carries 14 marks*

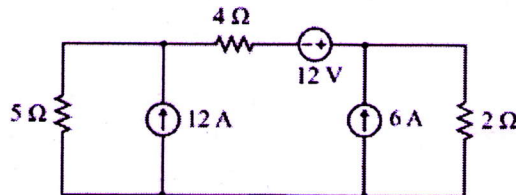**Module 1**

- 11 Apply superposition theorem to find the power dissipated in the  $5\Omega$  resistor in the circuit shown below. (14)




- 12 Obtain the Thevenin's and Norton's equivalent for the transistor amplifier circuit shown in the figure. (14)

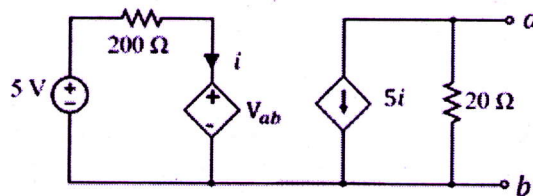


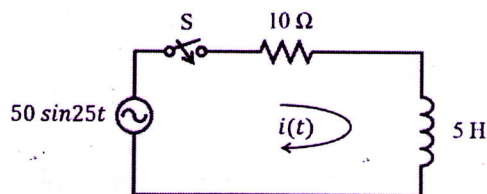**Module 2**


- 13 a) Using Laplace transform technique, determine the current  $I(s)$  in the network given below when the switch is closed at  $t = 0$ . Assume initially the inductor is relaxed. (4)



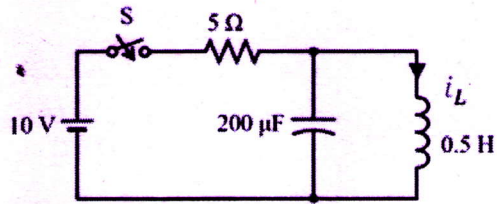- b) In the network shown in figure below, initially the switch S is closed and steady state is obtained. At  $t = 0$ , switch S is opened. Using Laplace transform technique, determine the current  $i_L(t)$  through the inductor. (10)




- 14 In the circuit given below, obtain  $i_L(t)$  when
- (a) Switch S is initially open and closed at  $t = 0$ . (8)
- (b) Switch S is initially closed and opened at  $t = 0$ . (6)

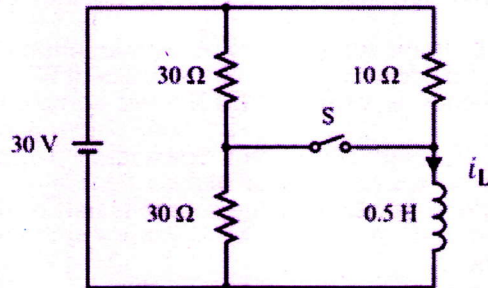


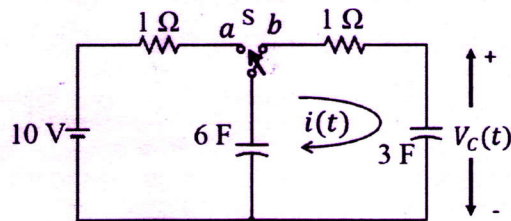**Module 3**

- 15 In the network, the switch S initially at position  $a$  for a long time, is changed to position  $b$  at time  $t = 0$ . Draw the transformed circuit and determine  $i(t)$  and  $V_c(t)$ . (14)




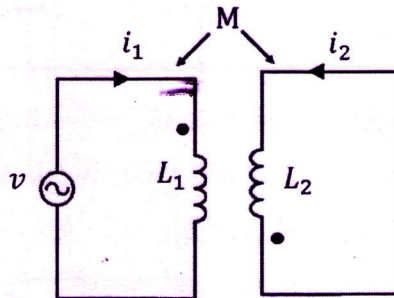- 16 a) Determine  $i_1(t)$  and  $i_2(t)$  in the circuit shown below if,  $L_1 = 0.4$  H,  $L_2 = 0.4$  H,  $v(t) = 15 \cos t$ , and  $M = 0.2$  H. (6)



- b) For the network shown below, find the voltage across 10 Ω resistor. (8)



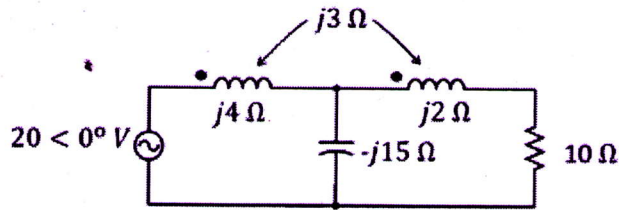


**Module 4**


- 17 A three-phase, 400 V RYB system, has a delta-connected load with  $Z_{RY} = 10 \angle 90^\circ \Omega$ ,  $Z_{YB} = 20 \angle 45^\circ \Omega$ , and  $Z_{BR} = 40 \angle -45^\circ \Omega$ . Calculate the phase currents, line currents and total power. Assume positive phase sequence. (14)
- 18 In an RLC series circuit supplied at 250 V, maximum current of 1 A flows when the supply frequency is varied to 60 Hz and corresponding voltage across the inductor is 500 V. Find the circuit constants, Q-factor, bandwidth, and the frequencies at which power from the source is half of the power delivered at the resonant frequency. (14)

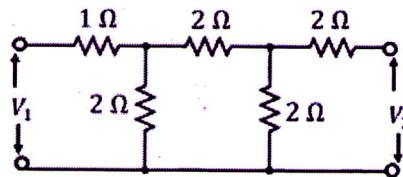**Module 5**


- 19 Obtain z-parameters for the circuit shown. Draw the z-parameter equivalent model and also find whether the network is reciprocal and symmetrical. (14)



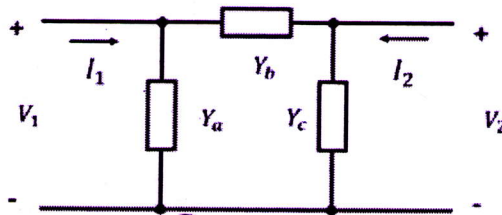- 20 a) For general  $\pi$ -network shown in the figure, obtain the y parameters. (6)



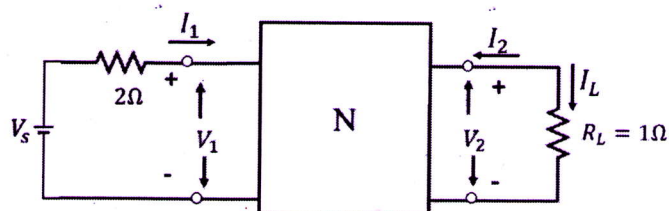- Find the value of source voltage  $V_s$  in the network shown. The power dissipated in the load resistance is 100 W and the network N is represented in terms of h parameters as  $h_{11} = h_{22} = 1$  and  $h_{12} = 2$ ,  $h_{21} = -2$ . (8)



\*\*\*\*\*