

C

0800RAT203122103


Pages: 3

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

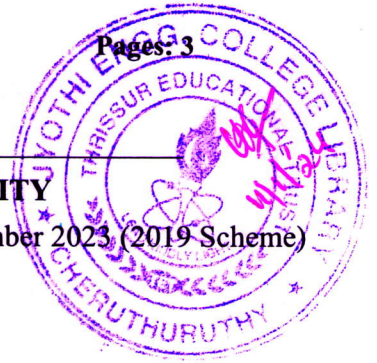Third Semester B.Tech Degree Regular and Supplementary Examination December 2023 (2019 Scheme)



Course Code: RAT203

Course Name: ELECTRONIC DEVICES AND CIRCUITS

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer all questions. Each question carries 3 marks*

Marks


- 1 Analyse the working of a combination clipper using diodes. (3)
- 2 Draw the h-Parameter model of a BJT. (3)
- 3 Illustrate the effect of Miller capacitance in the frequency response of a CS amplifier. (3)
- 4 Draw and explain the drain characteristics of JFET. (3)
- 5 Explain the working of Class C power amplifier. (3)
- 6 Compare positive feedback with negative feedback. (3)
- 7 State Bark Hausen's Criterion for sustained oscillations. (3)
- 8 How can op-amps be used to subtract two input voltages. (3)
- 9 Show that the output from a differentiating circuit is derivative of the input. (3)
- 10 Design a zero-crossing detector circuit using an op-amp. (3)

**PART B**

*Answer any one full question from each module. Each question carries 14 marks*

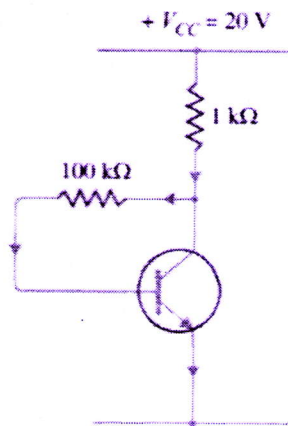**Module 1**

- 11 a What is the necessity of biasing circuits? With a neat circuit diagram derive the expression for stability factor for a fixed bias circuit. (7)
- b Consider the Collector feedback Resistor Bias circuit as shown in the figure below that has a silicon transistor with  $\beta=100$  and  $V_{BE}=0.7$  V. a) Find the operating point. b) Find the new operating point if  $\beta=50$  and all other circuit parameters remaining the same? (7)



- 12 a Sketch and explain the working of a positive shunt clipper to clip an input sinusoidal signal having peak values at  $\pm 6V$ , to a positive reference voltage of  $+2V$ . (4)
- b Explain the role of coupling and emitter bypass capacitors in amplifier circuits. (4)
- c Draw and explain the circuit for bias compensation using thermistor. (6)

#### Module 2

- 13 a With neat sketches explain the construction, working and characteristics of N-channel enhancement MOSFET. (8)
- b Explain voltage divider biasing scheme for JFET with the help of a neat sketch. (6)
- 14 a For a CS amplifier, draw the small signal equivalent circuit and determine the expression for gain, input impedance and output impedance. (10)
- b How can an FET act as a Voltage Controlled Resistance? (4)

#### Module 3

- 15 a Draw the circuit diagram and explain the working of a two stage RC Coupled amplifier. Also list its advantages and disadvantages. (8)
- b Explain the effect of negative feedback on gain, input impedance and bandwidth. (6)
- 16 a Explain the working of a Transformer coupled class A power amplifier with a neat circuit diagram. Derive the expression for maximum efficiency. (9)
- b With a neat schematic diagram explain the working of Direct coupled Transistor Amplifier. (5)

#### Module 4

- 17 a Analyse the working of an RC Phase shift oscillator with a neat diagram. Derive the expression for gain and frequency of oscillation. (10)
- b Design a non-inverting amplifier using op-amp. Derive the expression for its output voltage. (4)



- 18 a Explain the working of a crystal oscillator. (4)
- b Define the terms, CMRR and slew rate of an op-amp. Also specify their typical values for IC741. (5)
- c Design a summing amplifier circuit using op-amp to yield  $V_o = -V_1 + 2V_2 - 3V_3$ . (5)
- Assume the feedback resistance  $R_f$  as  $10\text{ K}\Omega$ .

**Module 5**

- 19 a With neat functional diagrams and relevant waveforms, Explain the working of Astable multivibrator using IC555 timer. (8)
- b Design a square waveform generator using op-amp for a frequency of 1KHz. (6)
- 20 a Draw and explain the circuit of a Schmitt trigger circuit using op-amp. Explain the terms UTP and LTP of a Schmitt trigger. (7)
- b Explain the principle of operation of a PLL IC 565 with the help of a block diagram. (7)

\*\*\*\*\*