

Reg No.: _____

Name: _____

0200ECT202122301

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S4 (S, FE) / S2 (PT) (S) Examination January 2024 (2019 Scheme)



Course Code: ECT202

Course Name: ANALOG CIRCUITS

Max. Marks: 100

Duration: 3 Hours

PART A

(Answer all questions; each question carries 3 marks)

Marks

- | | | |
|----|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|
| 1 | Derive the output voltage expression for an RC differentiator. | 3 |
| 2 | What is the need for biasing a transistor? What factors are to be considered for selecting the operating point Q? | 3 |
| 3 | Explain the hybrid- π parameters of BJT in CE configuration. | 3 |
| 4 | State Miller's theorem. | 3 |
| 5 | Draw the block diagram of a multistage amplifier with n number of stages and give an expression for its overall voltage gain. | 3 |
| 6 | Explain with a diagram common source MOSFET stage with diode-connected load | 3 |
| 7 | List any three advantages of negative feedback in amplifiers. | 3 |
| 8 | A voltage series negative feedback amplifier has a voltage gain without feedback $A = 500$. Input and output resistances are $3 \text{ K}\Omega$ and $20 \text{ K}\Omega$ respectively, feedback factor $\beta = 0.01$. Calculate the voltage gain A_f , R_{if} , R_{of} of the amplifier with feedback. | 3 |
| 9 | With the help of a block diagram explain the working of a linear regulated power supply. | 3 |
| 10 | Compare class A, class B, and class AB power amplifiers. | 3 |

PART B

(Answer one full question from each module, each question carries 14 marks)

Module -1

- | | | |
|----|--------------------------------------------------------------------------------------------------------------------------------------------------------------|---|
| 11 | a) Design an RC low pass filter with a cut off frequency 2 KHz. Also plot its frequency response. | 7 |
| | b) Explain the concept of operating point with help of dc and ac load lines. | 7 |
| 12 | a) Set up a slicer circuit that clips an input sine wave at +3V and -4V. Draw the output waveform and transfer characteristics. Assume the diodes are ideal. | 6 |

0200ECT202122301


- b) Derive the stability factor of a voltage divider bias circuit. 8

Module -2

- 13 a) Obtain the hybrid- π model for a single transistor with a resistive load R_L . 6
b) Short circuit CE current gain of transistor is 25 at a frequency of 2 MHz if $f_\beta = 200$ kHz. Calculate (i) f_T (ii) h_{fe} (iii) $|A_i|$ at a frequency of 10 MHz and 100 MHz 8
- 14 a) Explain the need of various components in an RC coupled amplifier with a neat circuit diagram, also draw its frequency response. 7
b) With a neat diagram explain high frequency equivalent circuit of BJT. 7

Module -3

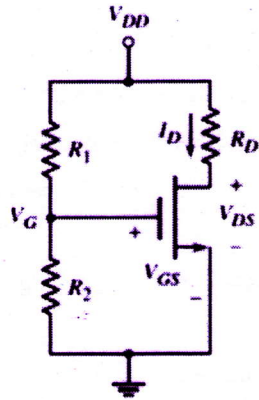- 15 a) Briefly explain the Common Source stage with current source load. 7
b) Draw the circuit of cascade amplifier and list any three advantages of this configuration. 7
- 16 a) Calculate the drain current and drain-to-source voltage of the following common source circuit. Given $R_1 = 15$ K, $R_2 = 10$ K, $R_D = 5.6$ K, $V_{DD} = 8$ V, $V_T = 1$ V, $K_n = 0.1$ mA/V². 7



- b) Explain any two biasing techniques for enhancement MOSFET. 7

Module -4

- 17 a) In a Wein bridge oscillator given that $R_1 = R_2 = 200$ K Ω and $C_1 = C_2 = 250$ pF. Determine the frequency of oscillations. 6
b) What are the four basic feedback topologies? Explain with block diagrams. 8
- 18 a) Explain the working principle of crystal oscillator. Draw the equivalent circuit of a crystal. 6

0200ECT202122301

- b) An amplifier has a voltage gain of 400, $f_1 = 50\text{Hz}$, $f_2 = 200\text{KHz}$ and a distortion of 10% without feedback. Determine the amplifier voltage gain, f_{1f} , f_{2f} and D_f when a negative feedback is applied with feedback ratio of 0.01. 8

Module -5

- 19 a) Explain the working of a transformer coupled class A power amplifier 8
b) Define line regulation and load regulation in a voltage regulator. 6
- 20 a) In a class B amplifier $V_{CEmin} = 2\text{V}$, supply voltage $V_{CC} = 15\text{V}$. Find the collector circuit efficiency η . 6
b) Describe the operation of a transistor shunt regulator. 8
