

D

0300ECT322052201

Pages: 2

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S6 (S, FE) / S4 (PT) (S) Examination January 2024 (2019 Scheme)



Course Code: ECT322

Course Name: POWER ELECTRONICS

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 3 marks.

- | | | Marks |
|----|--|-------|
| 1 | The reverse recovery time of a diode is $3\mu\text{s}$ and rate of fall of diode is $30\text{A}/\mu\text{s}$. Find stored charge and peak reverse current | (3) |
| 2 | Draw the static characteristics of SCR and define latching and holding current | (3) |
| 3 | What is the purpose of base drive circuit in power BJT? | (3) |
| 4 | For a single phase full wave controlled rectifier, draw the load voltage and current waveform for RLE load and give expression for average load voltage | (3) |
| 5 | What is the purpose of using freewheeling diode in converters? | (3) |
| 6 | What are benefits of isolated converters? | (3) |
| 7 | What is the significance of doing Fourier analysis in inverter output? | (3) |
| 8 | Distinguish between driven and self driven inverters | (3) |
| 9 | Illustrate the four quadrant operation of DC motor | (3) |
| 10 | How converters are used in electric welding? | (3) |

PART B

Answer one full question from each module, each carries 14 marks.

Module I

- 11 a) Explain the basic construction details, various modes of operation of GTO with its VI characteristics (10)
- b) Draw the gate current waveform of GTO and define backporch in GTO (4)

OR

- 12 a) Explain the principle of SCR with the help of its two-transistor model (7)
- b) Draw the basic structure and explain the working of IGBT (7)

Module II

- 13 a) Explain shunt snubber with the help of a diagram and derive the expression for the value of capacitor and range of resistor. (7)
- b) Design any two gate drive circuits for power MOSFET (7)

OR

- 14 a) Illustrate the operation of a single phase, 2 pulse fully controlled rectifier for RL load with circuit diagram and output voltage and current waveforms. Also plot voltage across thyristors during their ON and OFF states. (10)
- b) Derive the expression for average load voltage in the circuit (4)

Module III

- 15 a) Explain the operation of Buck convertor with the circuit diagram along with inductor and capacitor current waveform. (10)
- b) The buck regulator has an input voltage of 12 V. the required average output voltage is 5V at $R = 500 \text{ ohm}$. The peak to peak output ripple voltage is 20mV. the switching frequency is 25Kz. If the peak-peak ripple current of inductor is limited to 0.8A. Find a) duty cycle b) filter inductance c) filter capacitance d) critical inductance (4)

OR

- 16 a) Illustrate the working of forward converter and push pull converter with suitable circuit diagram and necessary waveforms (14)

Module IV

- 17 a) Illustrate the operation of a 3-phase inverter of 180° conduction mode with circuit diagram and waveforms (Phase voltage and line voltage) (8)
- b) Explain sinusoidal pulse width modulation in three phase inverters (6)

OR

- 18 a) What is space vector modulation in three phase inverters (7)
- b) Explain the operation of full bridge inverter (7)

Module V

- 19 a) Explain the principle of adjustable speed DC drive using switched mode DC-DC converter (8)
- b) Explain different braking mechanism in DC motor (6)

OR

- 20 a) Illustrate the principle of operation of variable frequency PWM – VSI Induction Motor Drive (7)
- b) Mention the industrial application of power electronics (7)
