

QP CODE:

Reg No: \_\_\_\_\_

Name: \_\_\_\_\_



APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

SECOND SEMESTER M.TECH DEGREE EXAMINATION, JUNE 2024

Course Code: 222EEE071

Course Name: **ELECTRIC CHARGING SYSTEMS FOR ELECTRIC VEHICLES**

Max. Marks : 60

Duration: 2Hrs 30 Minutes

**PART A**

**Answer All Questions. Each Question Carries 5 Marks**

1. What is a two quadrant chopper? Explain. (5)
2. What is inverted mode of operation of the converter? Explain. (5)
3. Draw and explain the configuration of a level-1 charger. (5)
4. Explain about the battery management systems used in EV. (5)
5. Explain the CHAdeMo charging protocol for EV. (5)

**Part B**

**(Answer any five questions. Each question carries 7 marks)**

6. Draw the circuit of 3 phase fully controlled rectifier with RL load and explain the working for  $\alpha=60$  degree with necessary waveforms. Derive the expression for average output voltage. (7)
7. Draw the circuit of 3 phase fully controlled rectifier with RLE load and explain the working for  $\alpha=600$  with necessary waveforms. Derive the expression for average output voltage. (7)
8. Explain about Types of charging stations - AC Level 1 & 2. (7)
9. Explain the operation of level-3 battery charger with a neat circuit diagram. (7)
10. Explain the working of a Buck-Boost regulator, showing relevant waveforms and derive the expression for its output voltage. (7)
11. Explain about Fuel cell based energy storage systems. (7)
12. Describe the various charging standards used for electric vehicles. (7)

\*\*\*\*\*