

Course Code: EC201

Course Name: NETWORK THEORY


Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks.

1 a)

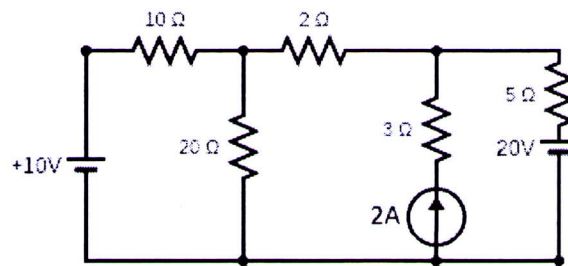

Marks


(10)

Determine the voltage across 2 Ω resistor using super-position theorem.

b) Illustrate the concept of source transformation with necessary sketches.

(5)

2 a)

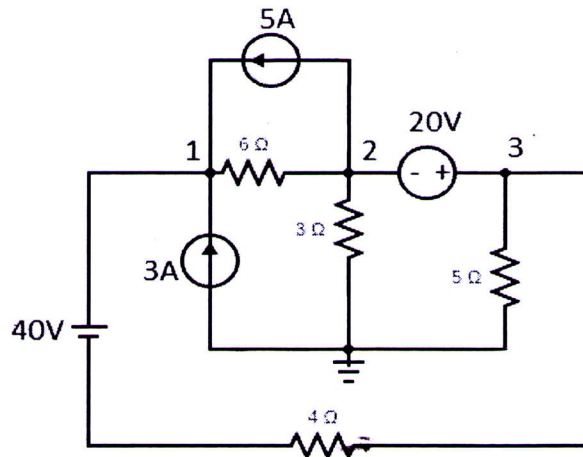

(10)


Determine the power dissipated by the 5 Ω resistor in the circuit.

b) State and prove maximum power transfer theorem

(5)

3 a)


(8)

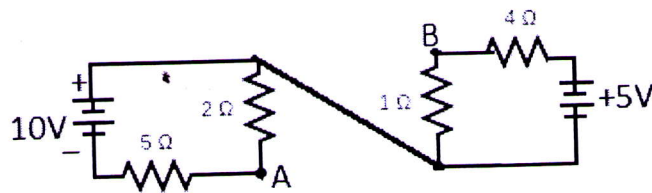

Determine the Thevni's equivalent circuit across terminals AB for the given circuit.

b)

(7)

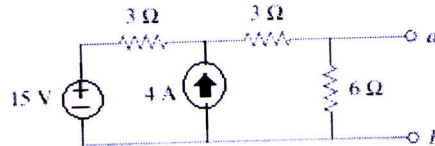


Using Norton's theorem, find R_N and I_N of the circuit across terminals a-b.

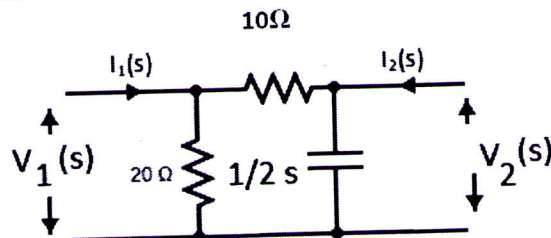PART B

Answer any two full questions, each carries 15 marks.

- 4 a) Determine the inverse Laplace transform of the function $G(s) = \frac{7}{(s^2 + 3)} + \frac{8}{(s + 5)}$ (6)
- b) Derive the response of a series RC circuit for a step input (6)
- c) Define poles and zeros of a transfer function (3)
- 5 a) Determine the transfer function $G_{21}(s)$, $Z_{21}(s)$ and driving point impedance $Z_{11}(s)$ of the given network (10)




- b) Draw the pole zero diagram for the transfer function $G(s) = \frac{4s(s+2)}{(s+1)(s+3)}$ (5) and also calculate $g(t)$.
- 6 a) Determine the solution of the following differential equation using Laplace transform method. (15)
- $$2y'' + 3y' - 2y = 2te^{-2t}$$
- $$y(0) = 0 \text{ and } y'(0) = -2$$

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) A series RLC circuit has the following parameter values $R=10\Omega$, $L=0.01H$, $C=100\mu F$. Compute the resonant frequency, lower and upper frequencies of the bandwidth. (8)

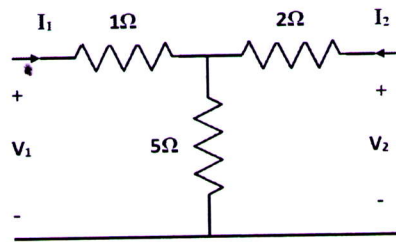- b) Find the transmission parameter for the network shown below (8)



- c) Obtain the condition for symmetry in two port networks. (4)
- 8 a) Express Z-parameter in terms of Y parameter and hybrid parameters (8)
- b) Compare series and parallel resonant circuit in terms of following parameters (8)
 (i) current at resonance (ii) impedance at resonance (iii) Power factor (iv) Quality factor
- c) A coil of 20Ω resistance has an inductance of 0.2 H and is connected in parallel with a condenser of $100\mu\text{F}$ capacitance. Find the value of dynamic resistance. (4)
- 9 a) Derive the expression for resonant frequency of a parallel RLC circuit. (8)
- b) Find the current through the capacitor in the given figure using mesh analysis. (12)

