

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

B.Tech Degree S5 (S, FE) / S3 (PT) (S, FE) Examination June 2024 (2015 Scheme)

**Course Code: EE305****Course Name: POWER ELECTRONICS**

Max. Marks: 100

Duration: 3 Hours

(Graph sheets may be supplied on demand)

**PART A***Answer all questions, each carries 5 marks.*

Marks

- |   |  |     |
|---|--|-----|
| 1 | Explain the working of thyristor using two-transistor analogy.   | (5) |
| 2 | Describe, using neat circuit diagram, the RC triggering circuit for SCR. Mention its one major advantage over R triggering.  | (5) |
| 3 | Explain and justify the theory of firing angle control for ideal dual converter  | (5) |
| 4 | Sketch the diagram and output voltage waveform of a single-phase half bridge Voltage Source Inverter with R load and describe the working.   | (5) |
| 5 | A single-phase full wave ac voltage controller (with two thyristors) has a resistive load of $10 \Omega$ and input voltage is 120 V (rms), 60 Hz. The delay angle of both thyristors is $\pi/2$ . Determine (i) rms output voltage (ii) input power factor (iii) average current of thyristors.  | (5) |
| 6 | Explain single-phase full bridge inverter using single pulse modulation technique of voltage control.  | (5) |
| 7 | With circuit diagram and waveforms, describe the working of Type-E chopper.  | (5) |
| 8 | A boost regulator has an input voltage of 5 V. The average output voltage is 15 V and average load current is 0.5 A. The switching frequency is 25 kHz. If inductance = $150 \mu\text{H}$ (in series with input side) and capacitance of $220 \mu\text{F}$ (parallel to output), determine (i) duty cycle (ii) ripple current of inductor $\Delta I$ . | (5) |

**PART B***Answer any two full questions, each carries 10 marks.*

- |   |  |     |
|---|--|-----|
| 9 | a) Explain neatly the structure, principle of operation and symbol of GTO.         | (5) |
|   | b) SCR with rating 1000 V and 200 A are available to be used in a string to handle | (5) |

- 6 kV and 1 kA. Calculate the number of series and parallel units needed, if the derating factor is 0.1 \*
- 10 a) Describe the variation of current and voltage during turn- on time of an SCR. (5)  
Sketch relevant switching characteristics for the explanation
- b) With the help of neat circuit diagrams, discuss 2 types of isolated gate (5)  
triggering circuits for a thyristor. Also compare these two.
- 11 a) A single phase fully controlled bridge rectifier supplies a RLE load. The (5)  
inductance L in the circuit is so large that the output current may be considered  
to be virtually constant. Assume ideal SCRs used.  
RMS supply voltage = 220 V, load resistance = 0.5  $\Omega$ , output dc current = 10  
A. Determine:  
(i) firing angle ( $\alpha$ ), if  $E = 135$  V  
(ii) Which source (ac or dc) is supplying power in the above case?
- b) Describe a single-phase half-controlled converter with RL load along with (5)  
necessary circuit diagram and waveforms.

### PART C

*Answer any two full questions, each carries 10 marks.*

- 12 Draw the circuit diagram and explain with necessary waveforms the working of (10)  
3-phase fully controlled rectifier with RLE load for firing angle  $\alpha = 60^\circ$ . Derive  
the expression for output voltage.
- 13 a) Explain advantages and disadvantages of circulating type dual converter with (5)  
that of non-circulating current type.
- b) Differentiate CSI from VSI. (5)
- 14 Draw the circuit and explain the operation of a 3-phase bridge inverter with R (10)  
load, operating in  $180^\circ$  conduction mode. Draw the output line voltage and  
phase voltage waveforms. Derive expressions for output line voltage and phase  
voltage.

### PART D

*Answer any two full questions, each carries 10 marks.*

- 15 a) Distinguish the terms amplitude modulation index and frequency modulation (5)  
index in sine PWM technique. How it affects the inverter output voltage.

- b) Explain, with circuit diagram and relevant waveforms, the working of two-stage sequence controller with R load. (5)
- 16 a) In a multiple-pulse modulation method, five pulses are generated per half cycle of the reference signal. If the supply voltage is 220 V (rms), calculate the pulse width for an output voltage of 160 V (rms). (5)
- b) Explain the working of a buck converter, with the help of a neat circuit diagram and waveforms of output voltage, inductor current and inductor voltage. (5)
- 17 a) A type-A chopper has dc source voltage 230 V, load resistance is  $10 \Omega$ . The voltage-drop across chopper during turn-on is 2 V. For a duty cycle of 0.4, calculate average and rms values of output voltage. (5)
- b) With the help of relevant waveforms, derive the expression for output voltage of a Buck-Boost converter in continuous conduction mode of operation. (5)

\*\*\*\*