

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S4 (S, FE) / S2 (PT) (S, FE) / S4 (WP) (S) Examination December 2024 (2019 Scheme)

Course Code: ECT202**Course Name: ANALOG CIRCUITS**

Max. Marks: 100

Duration: 3 Hours

PART A*(Answer all questions; each question carries 3 marks)***Marks**

- | | | |
|----|---|---|
| 1 | Design a circuit to obtain square wave output from triangular wave input with 5kHz frequency. | 3 |
| 2 | In a fixed bias circuit $R_B=560K\Omega$, $R_C=3k\Omega$. Let $V_{CC}=12V$, $\beta_{dc}=100$. Determine the value of operating point. Choose Si Transistor. | 3 |
| 3 | Define the small signal parameters g_m , r_e and r_π for a BJT amplifier. | 3 |
| 4 | Draw the dc and ac load line of RC coupled amplifier with bypass capacitor. | 3 |
| 5 | Compare BJT and MOSFET. | 3 |
| 6 | Discuss the common source MOSFET stage with diode-connected load. | 3 |
| 7 | Emitter follower is a Voltage series feedback amplifier. Justify the statement. | 3 |
| 8 | State and explain Barkhausen criteria for sustained oscillations | 3 |
| 9 | Compare various classes of Power amplifiers. | 3 |
| 10 | Discuss the principle of output current boosting in voltage regulator | 3 |

PART B*(Answer one full question from each module, each question carries 14 marks)***Module -1**

- | | | |
|----|--|---|
| 11 | a) Design a clamper circuit to get $V_o=10\sin(1000t) - 10V$. Draw its i/p and o/p wave | 7 |
| | b) What do you mean by thermal run away? How thermal stabilization is achieved in an RC coupled amplifier? Explain with neat sketches and equations. | 7 |
| 12 | a) Design a filter such that lower cutoff frequency equal to zero and upper cutoff frequency equal to 5kHz. | 7 |
| | b) Derive design equation of RC Differentiator. Show that output voltage is directly proportional to the derivative of input voltage. | 7 |

Module -2

- 13 a) Draw the high frequency hybrid - π equivalent circuit of a CE Amplifier and derive the expression for mid band gain and upper cut off frequency 9
- b) For an RC coupled amplifier with bypass capacitor, $R_1=100\text{ K}\Omega$, $R_2=20\text{ K}\Omega$, $R_C=3\text{ K}\Omega$, $R_E=1\text{ K}\Omega$ and $V_{CC}=12\text{ V}$. The β of the transistor is very high. Calculate the mid band gain of the amplifier. 5
- 14 a) For a CE amplifier with potential divider bias, $R_1=56\text{ K}\Omega$, $R_2=12.2\text{ K}\Omega$, $R_C=2\text{ K}\Omega$, $R_E=0.4\text{ K}\Omega$ and supply voltage $V_{CC}=10\text{ V}$. The signal source has a source resistance of $0.5\text{ K}\Omega$ and β of the transistor is given as 100. Calculate the small signal model parameters g_m , r_π and r_e and obtain the voltage gain, input impedance and output impedance of the amplifier. [A bypass capacitor is connected across the emitter resistor] 10
- b) State and explain Miller's Theorem. 4

Module -3

- 15 a) Calculate the drain current and drain-to-source voltage of a common source circuit with an n-channel enhancement mode MOSFET. Given: $R_1=22\text{ K}\Omega$, $R_2=10\text{ K}\Omega$, $R_D=6.8\text{ K}\Omega$, $V_{DD}=8\text{ V}$, $V_T=1\text{ V}$, $K_n=0.1\text{ mA/V}^2$. Also, calculate small signal voltage gain, input and output impedance. 8
- b) Why is the bandwidth of a cascode amplifier large when compared to Common source amplifier? 6
- 16 a) Derive small signal voltage gain, input and output resistance of Common source amplifier with constant current source. 9
- b) In an Enhancement MOSFET Voltage divider bias circuit threshold voltage (V_T)=2V and the drain current of 8 mA at a gate source voltage of 6 V. Calculate the drain current for a Q- point defined by $V_{GS}=4\text{ V}$ and $V_{DS}=10\text{ V}$. 5

Module -4

- 17 a) Explain the working of Wien bridge oscillator and derive feedback factor and frequency of oscillation. 9
- b) Design a Hartley oscillator to generate 1MHz sine wave. 5
- 18 a) Explain any two effects of negative feedback on amplifier performance. 7
- b) Determine the voltage gain, input and output resistance with feedback for voltage series feedback having $A=-100$, $R_i=10\text{ K}\Omega$ and $R_o=20\text{ K}\Omega$ for $\beta=-0.10$ 7

Module -5

- 19 a) Explain the working of Series voltage regulator. Deduce the expression for output voltage. 9
- b) With necessary sketches, discuss the fold-back protection in series voltage regulator. 5
- 20 a) Explain the working of a Transformer coupled Class A power amplifier and derive its maximum efficiency. 7
- b) Supply voltage of Complementary Symmetry Class B push pull power amplifier is +12 and -12V. If $R_L=8\ \Omega$, Calculate the maximum input power, maximum output power and maximum efficiency. 7
