

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

B.Tech S4 (Hons.) Degree Examination May 2025 (2023 Admn)

**Course Code: EET292****Course Name: NETWORK ANALYSIS AND SYNTHESIS**

Max. Marks: 100

Duration: 3 Hours

**PART A***(Answer all questions; each question carries 3 marks)*

Marks

- |   |   |   |
|---|---|---|
| 1 | Describe Tree, Co-Tree and Twig of a graph with proper examples                 | 3 |
| 2 | From the reduced incidence matrix given, draw the oriented graph of the network | 3 |

$$A = \begin{bmatrix} 1 & 0 & 0 & 1 & 0 & 1 & 0 \\ -1 & -1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & -1 & -1 & -1 & 0 & 0 \end{bmatrix}$$

- |   |  |   |
|---|--|---|
| 3 | What is meant by dual of a network graph to have a dual? Illustrate with an example. | 3 |
| 4 | What is meant by Tellegen's theorem  | 3 |
| 5 | Find the image impedances of the following two port network                          | 3 |

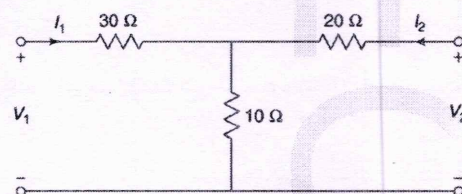


Figure 1

- |   |   |   |
|---|---|---|
| 6 | Classify the filters based on frequency characteristics                         | 3 |
| 7 | List the necessary and sufficient conditions for a function to be Positive Real | 3 |
| 8 |   | 3 |

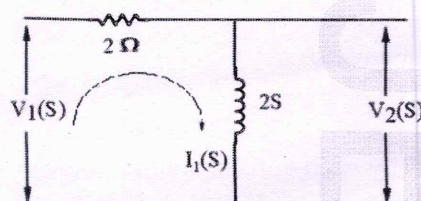


Figure 2



For the network shown in Figure 2, obtain the transfer functions  $G_{21}(S)$  and  $Z_{21}(S)$

- 9 Discuss the properties of LC immittance functions. 3
- 10 Determine whether following functions are RC impedance function or not. 3
- Justify your answer

$$(a) Z(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

$$(b) Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

### PART B

(Answer one full question from each module, each question carries 14 marks)

#### Module -1

- 11 a) Find all voltages and branch currents in the network shown in Figure 3 by node analysis, and applying network graph principles

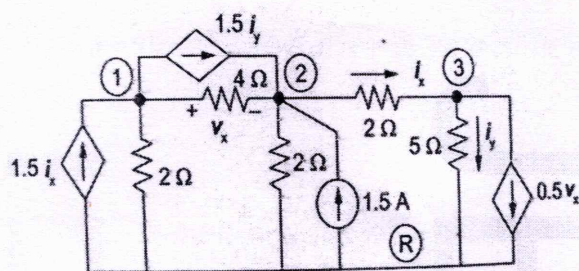


Figure 3

- b) For the circuit shown in Figure 4 draw the oriented graph and write the tie-set matrix

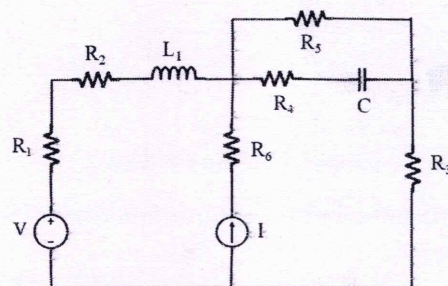


Figure 4

- 12 a) Determine the power delivered by each current source in the circuit given in Figure 5 by nodal analysis



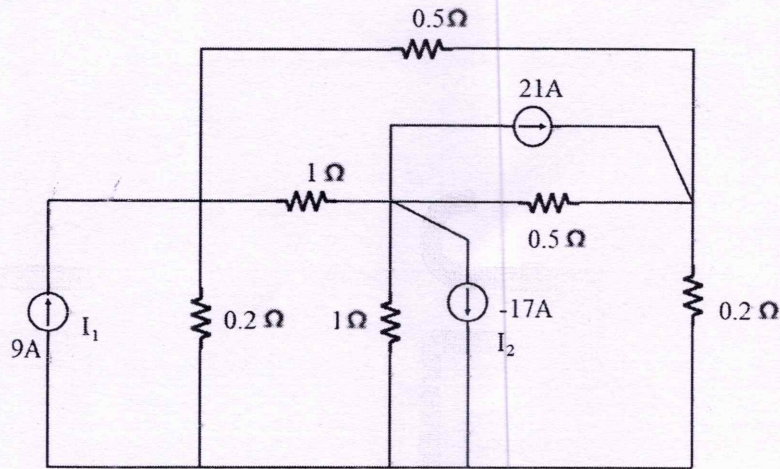


Figure 5

- b) For the network shown in Figure 6, obtain the incidence matrix and nodal admittance matrix

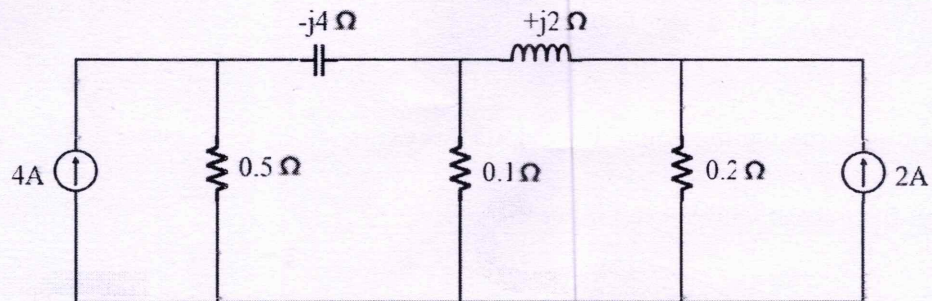


Figure 6

**Module -2**

- 13 a) Find the dual of the following circuits shown in Figure 7 and Figure 8 Show all intermediate steps

(i)

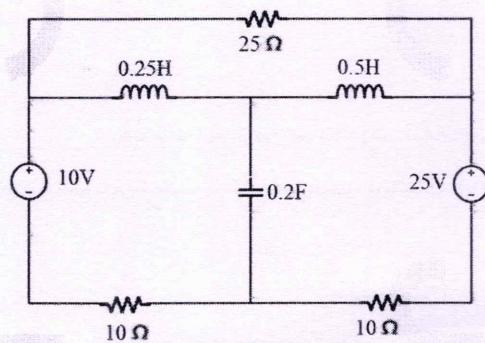


Figure 7



(ii)

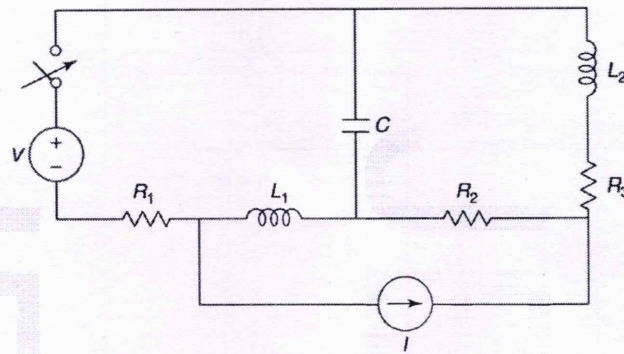


Figure 8

- b) Determine the  $B_f$  matrix for a graph with reduced incidence matrix

Branches: 1 2 3 4 5 6 7

$$A = \begin{matrix} \text{node-1} \\ \text{node-2} \\ \text{node-3} \end{matrix} \begin{pmatrix} -1 & 1 & 0 & 0 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 0 & -1 & 1 & -1 \end{pmatrix}$$

Without drawing the graph. Use  $\{2,3,5\}$  as twigs

- 14 a) For the network shown in Figure 9

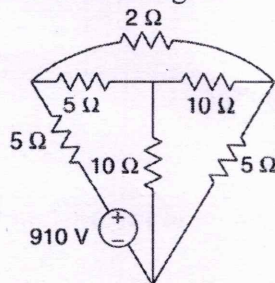


Figure 9

- a) Draw the oriented graph . 2  
 b) Obtain the f-cutset matrix 2  
 c) Calculate the twig voltages using KCL equation for the network 6  
 b) Obtain the relationship between circuit matrix , tie set matrix and incidence matrix 4

### Module -3

- 15 a) Design the T and  $\pi$  section of a constant K-type BPF with cut-off frequency of 4 kHz and 10 kHz and nominal characteristic impedance of 500  $\Omega$ . 7  
 b) Design an m-derived pi-section low-pass filter having cut-off frequency of 1500 Hz, design impedance of 500  $\Omega$  and infinite attenuation frequency of 2000 Hz. 7



- 16 a) 1. Design the T and Pi section of constant-k high pass filter having cut-off frequency of 10kHz and nominal characteristic impedance  $R_0 = 600 \Omega$ . 5  
 2. Find characteristic impedances and phase constant at 25kHz. 3  
 3. Find attenuation at 5kHz and 30kHz 2
- b) Design a T-type attenuator to give an attenuation of 60 dB and characteristic resistance of  $500 \Omega$  4

**Module -4**

- 17 a) Given  $I(s) = \frac{3s}{(s+1)(s+3)}$ . Draw the pole-zero diagram of the network function, 5  
 and hence, find time-domain response  $i(t)$ .
- b) State the conditions to be satisfied for a Hurwitz polynomial 3
- c) Test whether the polynomial  $P(s)$  is Hurwitz or not 6
- (i)  $P(s) = s^3 + 4s^2 + 5s + 2$
- (ii)  $P(s) = s^4 + s^3 + 3s^2 + 2s + 12$
- 18 a) Test whether  $F(s)$  is positive real function or not 8
- (i)  $F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$
- (ii)  $F(s) = \frac{s^2 + 4}{s^3 + 3s^2 + 3s + 1}$
- b) Find the limits of  $K$  so that the polynomial  $s^3 + 3s^2 + 2s + K$  6  
 may be Hurwitz.

**Module -5**

- 19 a) Realise the Cauer I and II forms of the following impedance function 10  

$$Z(s) = \frac{(s+2)(s+6)}{2(s+1)(s+3)}$$
- b) Obtain the Foster I form of the RL impedance function 4  

$$Z(s) = \frac{s(s+4)(s+8)}{(s+1)(s+6)}$$
- 20 Realise the impedance function  $Z(s)$  in three different ways 14  

$$Z(s) = \frac{4(s^2+1)(s^2+9)}{s(s^2+4)}$$

\*\*\*