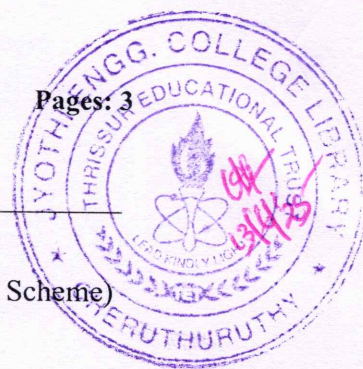


Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

B.Tech Degree S3 (S,FE) (FT/WP) (S1 PT) Examination May 2025 (2019 Scheme)

**Course Code: EET205****Course Name: ANALOG ELECTRONICS**

Max. Marks: 100

Duration: 3 Hours

**PART A***Answer all questions. Each question carries 3 marks*

Marks

- |    |   |     |
|----|---|-----|
| 1  | List down the factors affecting the stability of operating point of a transistor.                                 | (3) |
| 2  | Describe the role of emitter resistance in bias stabilisation.  | (3) |
| 3  | Illustrate how the different internal capacitances of BJT are incorporated in its high frequency hybrid pi model. | (3) |
| 4  | Define transconductance of JFET and derive its mathematical expression.   | (3) |
| 5  | State and explain Barkhausen criterion for feedback oscillators.  | (3) |
| 6  | Explain the terms (i) conversion efficiency and (ii) Harmonic distortion with respect to power amplifiers.        | (3) |
| 7  | Draw the basic block diagram of a general opamp and briefly explain the function of each block.                   | (3) |
| 8  | Realise a difference amplifier/ subtractor circuit using opamp and deduce the expression for output voltage.      | (3) |
| 9  | Give the detailed pin description of comparator IC LM311 and mention its salient features.                        | (3) |
| 10 | Explain the effect of slew rate on waveform generation.   | (3) |

**PART B***Answer any one full question from each module. Each question carries 14 marks***Module 1**

- |       |  |     |
|-------|--|-----|
| 11(a) | Derive an expression for stability factor for voltage divider bias of a BJT  | (7) |
| 11(b) | Calculate (i) input impedance $Z_{in}$ and (ii) voltage gain $A_v$ of the CE BJT amplifier shown in Figure (1). Given the h parameters of the transistor :<br>$h_{ie} = 1500\Omega$ , $h_{re} = 4 \times 10^{-4}$ , $h_{fe} = 100$ , $h_{oe} = 4 \times 10^{-4} S$ . | (7) |



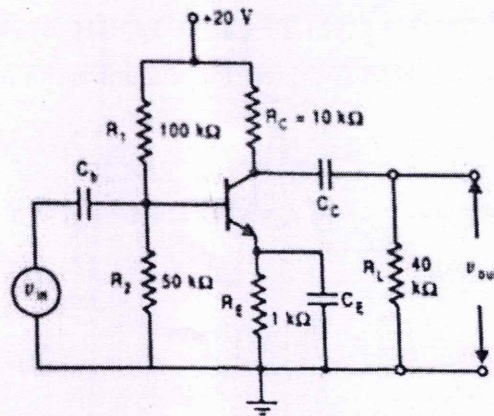


Figure (1)

- 12(a) Briefly explain Bias compensation using (i) diode and (ii) thermistors (7)
- 12(b) Derive the expressions for current gain, voltage gain, input impedance and output impedance in terms of h- parameters of BJT (7)

### Module 2

- 13(a) Explain the working of ENMOSFET with the help of its characteristic curves. (7)
- 13(b) Analyse the low frequency response of CE amplifier. (7)
- 14(a) Sketch the frequency response of CE amplifier and explain why gain falls at very high frequencies & very low frequencies. (7)
- 14(b) For the circuit shown in Figure (2), FET has  $I_{DSS} = 4 \text{ mA}$  and  $V_p = -4 \text{ V}$ . Calculate  $I_D$ ,  $V_{GS}$  and  $V_{DS}$ . (7)

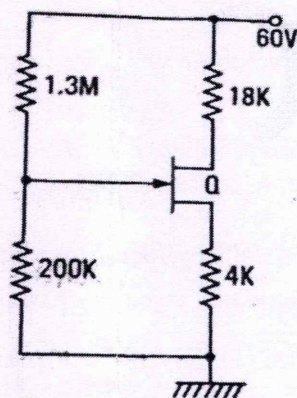


Figure (2)

### Module 3

- 15(a) Explain the working of two-stage transformer coupled amplifier with circuit diagram. (7)



- 15(b) Draw the circuit diagram of Colpitt's Oscillator and explain its principle of operation. (7)
- 16(a) Compare the merits and demerits of different types of inter stage coupling in amplifiers. (7)
- 16(b) Describe class A operation of power amplifiers and derive the expression for conversion efficiency of transformer coupled class A power amplifier. (7)

#### Module 4

- 17(a) Explain the different modes of operation of a fundamental differential amplifier. (7)
- 17(b) Define (i) CMRR and (ii) Slew rate. (7)  
Give the typical values of above parameters for 741 IC
- 18(a) Mention the salient features of an instrumentation amplifier. Derive the expression for its output voltage. (7)
- 18(b) Find the output voltage of the following op-amp circuit shown in Figure (3) (7)

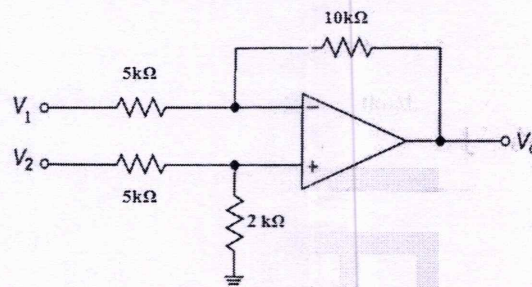


Figure (3)

#### Module 5

- 19(a) Explain the operation of op-amp integrator circuit. What practical modifications are to be incorporated into the basic integrator and why? (7)
- 19(b) Describe the operation of Schmitt trigger circuit. (7)
- 20 With the help of internal circuit diagram of IC555 explain the operation of astable multivibrator. Derive the expression for frequency of oscillation. (14)

\*\*\*