 


D 10050

(Pages : 2)

Name

Reg. No.



THIRD SEMESTER B.TECH. (ENGINEERING) DEGREE  
EXAMINATION, DECEMBER 2010

CS/IT 09 306/PTCS 09 305—SWITCHING THEORY AND LOGIC DESIGN

(2009 Admissions)

Time : Three Hours


Maximum : 70 Marks

Part A

Answer all questions.

Each question carries 2 marks.

 1. Convert  $(2142.53)_{10}$  to Octal and binary numbers.
2. Draw the logic diagram of a half adder and form the truth table.
3. Compare combinational and sequential circuits.
4. Determine a complete test set for the 3-input NAND gate as shown below :



5. With neat sketches and truth table explain about negative edge triggered D flip-flop.

(5 × 2 = 10 marks)

Part B

Answer any four questions.

Each question carries 5 marks.

6. State and prove De Morgan's theorems.
7. Implement the logic function  
$$Y = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$$
using 8 : 1 multiplexer.
8. Explain why NAND and NOR are called universal gates.
9. With a neat block diagram explain signature analysis.
10. What is meant by race around condition ? How can it be avoided ?
11. Show how SR flip-flop is converted to JK and D flip-flops.

(4 × 5 = 20 marks)

Part C

12. (a) Minimize the following functions using K-map :—
  - (i)  $F(A, B, C, D) = \sum m(5, 7, 8, 10, 13, 15) + \sum d(0, 1, 2, 3)$ .
  - (ii)  $Y = \pi m(0, 1, 4, 5, 6, 8, 9, 12, 13, 14)$ .

Or

Turn over

(b) Using Quine Mc Cluskey method minimize the following function —

$$F(A, B, C, D, E) = \sum m(0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31).$$

13. (a) Implement full subtractor using demultiplexer.

Or

(b) Design a code converter combinational circuit to convert binary to BCD.

14. (a) Write notes on PLA minimization.

Or

(b) Explain Boolean difference method for fault detection.

15. (a) Design Mod-10 counter using JK flip-flops and discuss.

Or

(b) Explain different types of shift register counters in detail.

(4 × 10 = 40 marks)