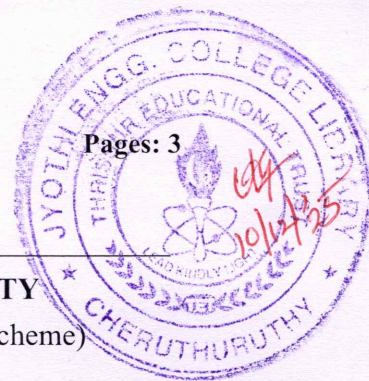


Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
 B.Tech Degree S3 (S,FE) Examination December 2025 (2019 Scheme)



**Course Code: RAT203**  
**Course Name: ELECTRONIC DEVICES AND CIRCUITS**

Max. Marks: 100

Duration: 3 Hours


**PART A***Answer all questions. Each question carries 3 marks*

- |  | Ma<br>rks |
|--|-----------|
| 1 Distinguish between series and shunt positive clippers.  | (3)       |
| 2 Draw the low frequency equivalent circuit of a BJT.  | (3)       |
| 3 How can an FET be used as a switch.  | (3)       |
| 4 Draw the Hybrid Pi model of BJT amplifier and list the parameters.   | (3)       |
| 5 What are the two different feedback arrangements used in electronic circuits?  | (3)       |
| 6 Analyse the effect of negative feedback on the gain of the amplifier.  | (3)       |
| 7 Explain the basic principle of LC Oscillators.   | (3)       |
| 8 Calculate the output voltage of an inverting amplifier with an input of 10V, $R_1=10\text{ K}\Omega$ , $R_f=10\text{ K}\Omega$ . Assume an ideal op-amp. | (3)       |
| 9 Draw the functional block diagram 555 Timer IC.  | (3)       |
| 10 Illustrate the circuit of a 78XX IC based voltage regulator.  | (3)       |

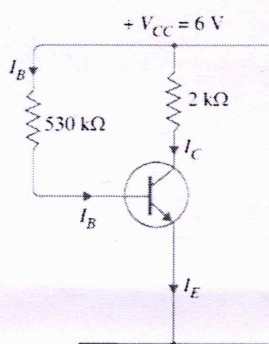**PART B***Answer any one full question from each module. Each question carries 14 marks***Module 1**

- 11 a Identify the need for biasing in electronic circuits. With a neat circuit diagram and relevant equations explain voltage divider bias for a common emitter configuration. (8)
- b Consider the Fixed Bias circuit as shown in the figure below that has a silicon transistor with  $\beta=50$ ,  $V_{CC}=6\text{V}$ ,  $R_C=2\text{K}\Omega$ ,  $R_B=530\text{ K}\Omega$ ,  $V_{BE}=0.7\text{V}$ . Draw the DC load line and determine the operating point and stability factor. (6)





- 12 a Draw and explain the circuit for bias compensation using diode. (7)
- b Analyse the working of a Zener diode shunt regulator with the help of a circuit diagram. (4)
- c Define stability factor. Write down the expression for stability factor S. (3)

### Module 2

- 13 a Explain the constructional details and characteristics of a JFET with neat diagrams. (8)
- b Select a suitable biasing scheme for MOSFET amplifiers. (6)
- 14 a Enumerate on low frequency analysis of BJT Common Emitter amplifier. (8)
- b Briefly explain about Miller effect capacitance. (6)

### Module 3

- 15 a Draw the circuit diagram and explain the working of a Transformer Coupled amplifier. Also list its advantages and disadvantages. (8)
- b Draw a negative voltage series feedback topology and derive the expression for its output impedance. (6)
- 16 a Explain the working of a class B power amplifier with a neat circuit diagram. Derive the expression for maximum efficiency of a class B power amplifier. (8)
- b Briefly explain the three types of coupling methods used in multistage amplifiers. (6)

### Module 4

- 17 a With a neat schematic explain the working of Colpitts oscillator and derive the expression for its frequency of oscillation. (8)
- b Draw an Adder-Subtractor circuit using a single op-amp and derive the expression for the output voltage. (6)
- 18 a With a neat circuit diagram explain the working of a Wein bridge oscillator and derive its frequency of oscillation. (8)
- b With the help of a diagram explain a three input inverting summing amplifier. (6)

### Module 5

- 19 a With a neat circuit diagram and relevant waveforms, explain the working of a monostable multivibrator using IC555 timer. (8)
- b Draw the internal schematic of IC723 and explain its working. (6)
- 20 a Explain with a neat circuit diagram the working of a triangular waveform generator using op-amp. (7)
- b Draw the block schematic of PLL IC 565 and describe the function of each block. (7)

\*\*\*