

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
B.Tech Degree S1(S) Examinations May 2026 (2024 Scheme)



Course Code: GXEST104

**Course Name: INTRODUCTION TO ELECTRICAL AND ELECTRONICS
ENGINEERING**

Max. Marks: 60

Duration: 2 hour 30 minutes

- Use separate answer sheets for Part 1 and Part 2
- No separate minimum marks are required to pass.

PART 1: ELECTRICAL ENGINEERING (30 Marks)

**PART 1-A
Module (1 & 2)**

Answer all questions. Each question carries 3 marks

		CO	Marks
1	State Kirchoff's laws in an electric circuit.	1	3
2	Compare series and parallel magnetic circuits	2	3
3	Derive the expression for coupling coefficient K in a coupled circuit. What are the indications for the following values of K , (i) $K = 0$ and (ii) $K = 1$?	1	3
4	Show that the average power absorbed by a pure capacitive load is zero.	1	3

**PART 1-B
Module (1&2)**

Answer any one full question from each module. Each question carries 9 marks

Module 1

- | | | | |
|---|---|---|---|
| 5 | a) Differentiate between statically induced emf and dynamically induced emf with an example for each. | 1 | 3 |
| | b) Apply Kirchoff's laws to find the currents I_1 , I_2 and I_3 in the circuit shown in figure (1). | 1 | 6 |

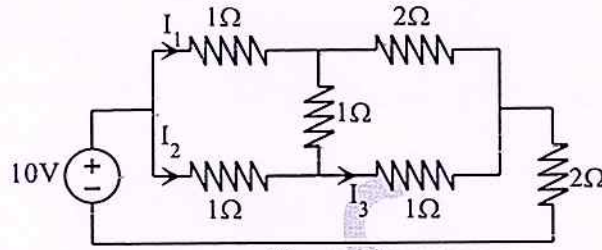


Figure (2)

- | | | | |
|---|--|---|---|
| 6 | a) Derive the expression for energy stored in an inductor. | 1 | 3 |
| | b) Determine the mesh currents in the circuit of Figure 2. | 1 | 6 |

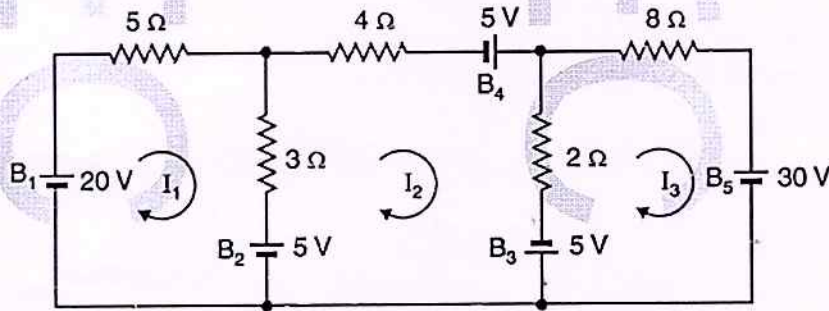


Figure 2

Module 2

- | | | | |
|---|---|---|---|
| 7 | a) The instantaneous value of a voltage is given as $v(t) = 100\sin 377t$ volts. Determine its frequency, time period, RMS value, average value, form factor and peak factor. | 1 | 4 |
| | b) A series RLC circuit with $R = 4\Omega$, $X_L = 5\Omega$ and $X_C = 2\Omega$ is supplied from a 50V supply. Find the impedance, power factor and current drawn from the supply. Also find the voltage across R, L and C. | 1 | 5 |
| 8 | a) State and explain Faraday's laws of electromagnetic induction. | 1 | 4 |
| | b) A 3-phase 100V, 50Hz balanced supply is connected to a balanced 3-phase delta-connected R-L load with $R = 5\Omega$ and $L = 0.01H$. Find the current drawn from the supply and the current flowing through each phase of the load. Also draw the phasor diagram. | 3 | 5 |

PART 2: ELECTRONICS ENGINEERING (30 Marks)**PART 2-A
Module (3 & 4)***Answer all questions. Each question carries 3 marks*

		CO	Marks
1	Derive the ripple factor of a full wave rectifier without filter .	4	3
2	Explain the process of avalanche breakdown..	4	3
3	What is the need for modulation?	5	3
4	Explain the general block diagram of communication system.	5	3

**PART 2-B
Module (3 & 4)***Answer any one full question from each module. Each question carries 9 marks***Module 3**

5	a) Explain the construction and working of an N-channel MOSFET.	4	5
	b) Explain with a neat circuit diagram how a Zener diode can be used as a voltage regulator.	4	4
6	a) Explain the input and output characteristics of BJT in Common Emitter configuration.	4	6
	b) Explain why the gain of an RC-coupled amplifier falls at high and low frequencies.	4	3

Module 4

7	a) Draw the block diagram and explain the principle and working of an FM superheterodyne receiver.	5	5
	b) Describe the functions of various components of Network Switching System in GSM.	5	4
8	a) Draw the block diagram of a digital multimeter and explain.	6	5
	b) Draw the block diagram of a function generator and explain.	6	4
