

FOURTH SEMESTER B.TECH (ENGINEERING) DEGREE EXAMINATION
DECEMBER 2010

EE 2K 404/PTEE 2K 302 - ELECTRONICS - II

Time : Three Hours



PART - A

- I
- Show the advantages of negative feedback in a single time constant voltage to voltage amplifier with respect to Bandwidth and rise time.
 - What do you understand by pole migration of right of s-plane in feedback amplifiers? State the need.
 - Distinguish between internally compensated and externally compensated of Amps.
 - Draw and explain the circuit of V-I converter with grounded load and discuss any one of its application.
 - Draw the block diagram of IC ICL8038 function generator and state function of each block.
 - Explain the application of PLL as frequency demodulator.
 - Explain the circuit of an analog switch.
 - Compare weighted Resistor DAC, R/2R ladder DAC, current switching DAC, multiplying DAC based on accuracy, linearity, monotonicity and area. (8×5 = 40)

PART - B

- II a) Discuss the characteristics of voltage shunt negative feedback amplifier with respect to gain, input and output resistances, Bandwidth, nonlinearity and stability
- (OR)
- b) i) Write a note on stability of feedback amplifiers.
ii) Draw the circuit of RC phase shift oscillator and obtain expression for frequency of oscillation and condition for sustained oscillation
- III a) i) Explain the output stage of LM741 op Amp
ii) Why is an opAmp integrator called lossy? Explain how it can be overcome with relevant diagrams.
- (OR)
- b) Discuss the features of instrumentation amplifier with circuit.
- IV a) With circuit schematic explain the following
- Precision Full Wave Rectifier
 - Op Amp based Astable Multivibrator
- (OR)
- b) Discuss the features of PLL and derive expressions for lock and capture range.
- V a) i) Design a wide-band pass filter having $f_l = 400 \text{ Hz}$, $f_h = 2 \text{ KHz}$ and pass-band gain of 4. Find the value of Q of the filter.
ii) Compare Butterworth and Sallen-key filters.
- (OR)
- b) Explain the architecture of dual slope ADC and compare with single slope ADC. (4×15 = 60)