

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
B.Tech Degree S6 (R,S) Examinations April 2026 (2019 Scheme)



Course Code: ECT312
Course Name: DIGITAL SYSTEM DESIGN

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 3 marks.

Marks


- | | | |
|----|---|-----|
| 1 | Discuss the key differences between synchronous and asynchronous sequential circuits. | (3) |
| 2 | Briefly explain three state assignment methods that can be used in the design of clocked synchronous sequential circuits with examples. | (3) |
| 3 | Describe the concept of a merger diagram and illustrate it with an example | (3) |
| 4 | With examples, differentiate between critical and non-critical race conditions in asynchronous sequential circuits. | (3) |
| 5 | Distinguish between static and dynamic hazards in digital circuit design. | (3) |
| 6 | Explain the concept of clock skew and mention any two factors responsible for it. | (3) |
| 7 | Briefly describe any three test pattern generation approaches for BIST. | (3) |
| 8 | Define Automatic Test Pattern Generation (ATPG). State its purpose and importance in VLSI testing. | (3) |
| 9 | What is the role of the switch matrix in a CPLD? Explain with reference to the XC9500 family. | (3) |
| 10 | Describe the role of programmable interconnect in Xilinx XC4000 FPGA family. | (3) |

PART B

Answer one full question from each module, each carries 14 marks.


Module I

- | | | |
|----|---|-----|
| 11 | a) Design a sequence detector which generates an output $z=1$, whenever the string is 1101, and generates a '0' at all other times. The overlapping sequences are detected. Implement the Mealy model circuit using D FFs. | (9) |
| | b) Construct an ASM chart for the following state diagram shown. | (5) |

 

OR

 - 12 a) Analyze the following clocked synchronous sequential network. Construct the excitation table, transition table, state table and state diagram. (7)



- b) Using implication chart construct the minimal state table from the state table given below. (7)

PS	X = 0	X = 1	Z
A	G	C	0
B	F	H	0
C	E	D	1
D	A	C	0
E	C	A	1
F	F	B	1
G	A	C	0
H	C	G	1


Module II

- 13 a) Design an asynchronous sequential circuit with two inputs X and Y and an output Z. The output should go high when X = 1 and Y changes from 0 to 1, and stay high until Y returns to 0. (9)

 - b) Explain any one race free state assignment method in asynchronous sequential network with example. (5)

OR

- 14 a) Analyze the following asynchronous sequential circuit by forming the excitation/transition table, state table, flow table and flow diagram. The network operates in fundamental mode with the restriction that only one input variable can change value at a time. (8)



- b) Obtain the primitive flow table and minimal row flow table for a fundamental mode asynchronous sequential circuit with inputs P and Q and output R. When P = 1, output R should be 1 if Q = 0, and when P = 0, output R should stay constant. (6)

Module III


- 15 a) Given the SOP expression $F = \sum (1, 2, 3, 7)$, construct the corresponding logic circuit. Analyze the possibility of hazards in the circuit and explain how they can be removed. Draw the hazard free circuit. (9)
- b) What is switch bounce? Explain how a debouncing circuit using an SR latch helps to overcome the problem of switch bounce. (5)

OR

- 16 a) Analyze the Boolean expression $F = w'x + wx'y + xy$ for static-1 hazards. If detected, eliminate them using redundant terms and draw the hazard free circuit. (8)
- b) With the help of a neat timing diagram, explain the operation of a two-flip-flop data synchronizer. (6)

Module IV

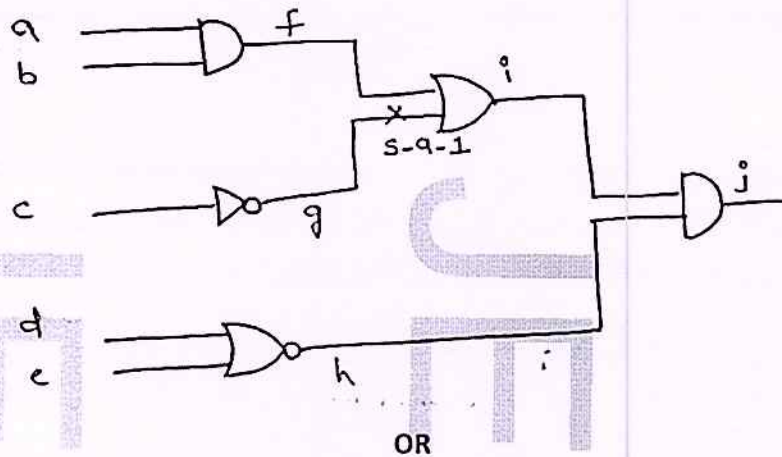- 17 a) Illustrate the fault table method used for effective test set generation for the circuit with the Boolean function $F = AB + A'C$. (8)
- b) Describe the path sensitization method for fault detection. Using path sensitization, find the test set for the fault SA1 at g in the following circuit. (6)



OR

- 18 a) Find the test vector of all SA0 and SA1 faults of the circuit whose Boolean function is $f = x_1 x_2 + x_1 x_3' x_4' + x_2 x_4$ by the Kohavi algorithm. (8)
- b) Describe the Boolean difference method for detecting faults with an example. (6)

Module V

- 19 a) Describe the input/output block (IOB) structure in the XC9500 CPLD family and explain how it supports different I/O standards with the help of a diagram. (7)
- b) Explain the structure of a configurable logic block (CLB) in the XC4000 FPGA. Discuss how CLBs are used to implement combinational and sequential logic. (7)

OR

- 20 a) Compare the XC9500 CPLD family with XC4000 FPGA in terms of architecture, flexibility, and typical applications. (6)
- b) Describe the architecture of the Xilinx XC4000 FPGA family with the help of a functional block diagram. (8)
