 




Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech Degree S5 (S,FE) (FT/WP/S3PT) Examinations June 2026 (2019 Scheme)

Course Code: ECT301

Course Name: LINEAR INTEGRATED CIRCUITS

Max. Marks: 100


Duration: 3 Hours

PART A

(Answer all questions; each question carries 3 marks)

Marks

- 1 Draw the equivalent circuit of a practical op-amp and list its four non ideal dc characteristics 3
- 2 A differential amplifier has common mode gain of 0.1 and difference mode gain of 500. Calculate output voltage for input signals $V_1=0.7\text{mV}$ and $V_2=0.4\text{mV}$ 3
- 3 Draw a half wave rectifier circuit to rectify an ac voltage of 0.2V. Explain the process of rectifying such a low signal 3
- 4 Find the output voltage for the circuit shown in figure 3

 

- 5 Design RC phase shift oscillator for a frequency of 2kHz 3
- 6 Design second order butterworth high pass filter with $f_L=2\text{kHz}$ 3
- 7 Draw the block diagram of frequency multiplier using PLL 3
- 8 Design a monostable multivibrator using 555 timer for a pulse period of 1ms 3
- 9 What is the significance of the reference voltage supply in IC 723? 3
- 10 Define the terms (a) Line regulation, (b) Load regulation and (c) Ripple Rejection 3

PART B

(Answer one full question from each module, each question carries 14 marks)

Module -1


- 11 a) Derive expression for differential gain, common mode gain, CMRR and differential input resistance for dual input unbalanced output differential amplifier 7
- b) Wilson current mirror is superior to normal current mirror. Establish mathematically 7
- 12 a) For dual input balanced output differential amplifier $R_C=2.2K$, $R_E=4.7K$, $V_{CC}=10V$, $V_{EE}=10V$. For the transistors have $\beta=100$ and $V=0.7V$. Determine (a) Q points (b) Differential voltage gain 10
- b) An op-amp 741 connected as a unit gain inverting amplifier having a slew rate of $0.5V/\mu s$. Determine the time taken for the output to change by $10V$ 4

Module -2

- 13 a) Explain the op-amp circuit for voltage shunt feedback. Derive the expression for closed loop gain, input resistance and output resistance. 7
- b) Explain the working of V to I converter with grounded load 7
- 14 a) Draw the circuit of instrumentation amplifier. Derive an expression for its differential gain 7
- b) Design Schmitt trigger for $UTP=2V$, $LTP= -2V$ 7

Module -3

- 15 a) Explain the working of wienbridge oscillator. Derive an expression for frequency of oscillation 7
- b) Design a square wave oscillator for $f_o=1kHz$ using 741 op-amp with dc supply voltage $\pm 12V$ and duty cycle 50% 7
- 16 a) Derive an expression for transfer function of first order LPF 7
- b) For the circuit shown in figure $R_1=100k\Omega$, $R_2=10k\Omega$, $R_3=20k\Omega$, $C_1=0.01\mu F$ and $\pm V_{sat}=\pm 14V$ for the op -amps. Determine (a) period, (b) peak value of square wave (c) peak value of triangular wave 7

 

Module -4

- 17 a) Design an astable multivibrator using 555 timer for a frequency of 1kHz and a duty cycle of 70%. Assume $C=0.1\mu\text{F}$ 7
- b) Draw the block diagram of PLL IC 565 and explain its operation 7
- 18 a) Determine the change in control voltage v_c during lock, if input signal frequency $f_s=20\text{kHz}$, the free running frequency is 21kHz and the V/F transfer coefficient of VCO is 4kHz/V. 7
- b) Define Capture range, lock range and pull in time of PLL 7

Module -5

- 19 a) What is fold back current limiting? Draw a regulator circuit with this implementation 7
- b) With block diagram describe the working of successive approximation ADC 7
- 20 a) Draw the circuit diagram of an n bit weighted resistor DAC. Explain its operation. 7
- b) A system employs a 16 bit word for representing an input signal. If the maximum output voltage is set to 2V, calculate resolution of the system and its dynamic range 7
